

COMP3211 03S2 Lecture 20

Single Cycle Datapath Control

Adapted from

CS152: Computer Architecture and Engineering
Dave Patterson (www.cs.berkeley.edu/~pattsrn)


Copyright 1997 UCB

Recap: Summary from last time

- 5 steps to design a processor
 - 1. Analyze instruction set => datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that affect the register transfer.
 - 5. Assemble the control logic
- MIPS makes it easier
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates
- Single cycle datapath => CPI=1, CCT => long

Recap: The MIPS Instruction Formats

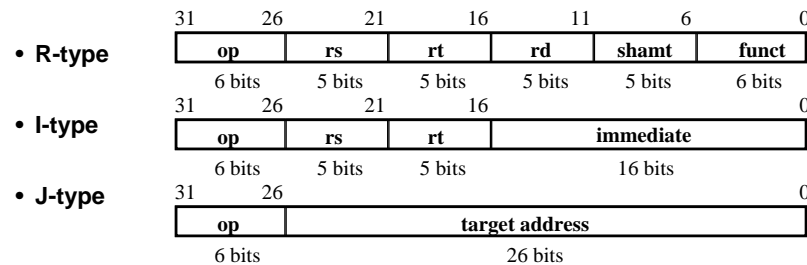
- All MIPS instructions are 32 bits long. The three instruction formats:



- The different fields are:
 - op: operation of the instruction
 - rs, rt, rd: the source and destination registers specifier
 - shamt: shift amount
 - funct: selects the variant of the operation in the “op” field
 - address / immediate: address offset or immediate value
 - target address: target address of the jump instruction

Recap: The MIPS Subset

 
- ADD and subtract
 - add rd, rs, rt
 - sub rd, rs, rt
- OR Imm:
 - ori rt, rs, imm16
- LOAD and STORE
 - lw rt, rs, imm16
 - sw rt, rs, imm16
- BRANCH:
 - beq rs, rt, imm16



Recap: A Single Cycle Datapath


- We have everything except control signals (underline)

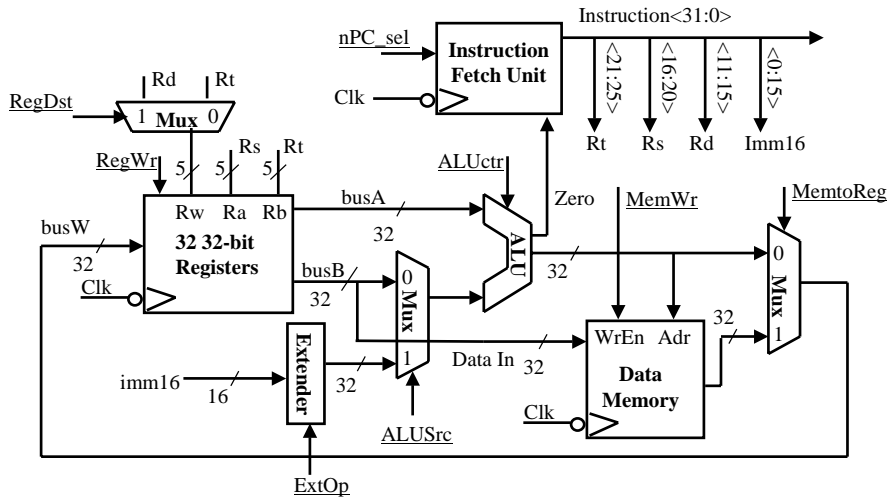Today's lecture will show you how to generate the control signals



The Big Picture: Where are We Now?

 - The Five Classic Components of a Computer




- Today's Topic: Designing the Control for the Single Cycle Datapath

Outline of Today's Lecture

- Recap and Introduction
- Control for Register-Register & Or Immediate instructions
- Control signals for Load, Store, Branch, & Jump
- Building a local controller: ALU Control
- The main controller
- Summary

RTL: The Add Instruction

 

- add rd, rs, rt

- mem[PC]

Fetch the instruction from memory

- $R[rd] \leftarrow R[rs] + R[rt]$


The actual operation

- $PC \leftarrow PC + 4$


Calculate the next instruction's address

Instruction Fetch Unit at the Beginning of Add

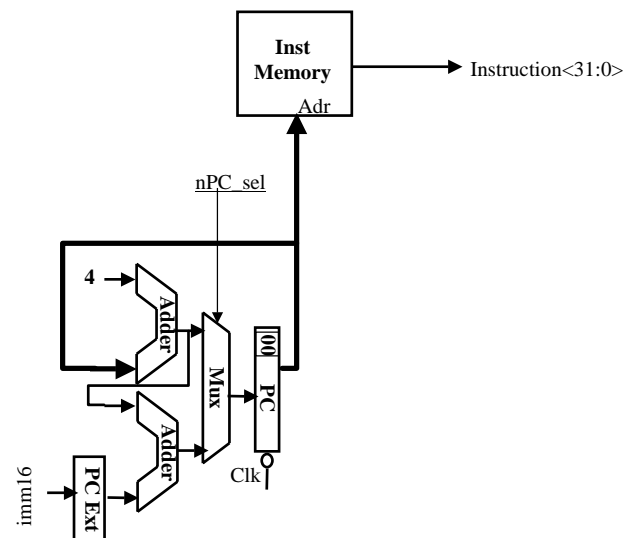- Fetch the instruction from Instruction memory: $\text{Instruction} \leftarrow \text{mem}[\text{PC}]$
 - This is the same for all instructions




The Single Cycle Datapath during Add

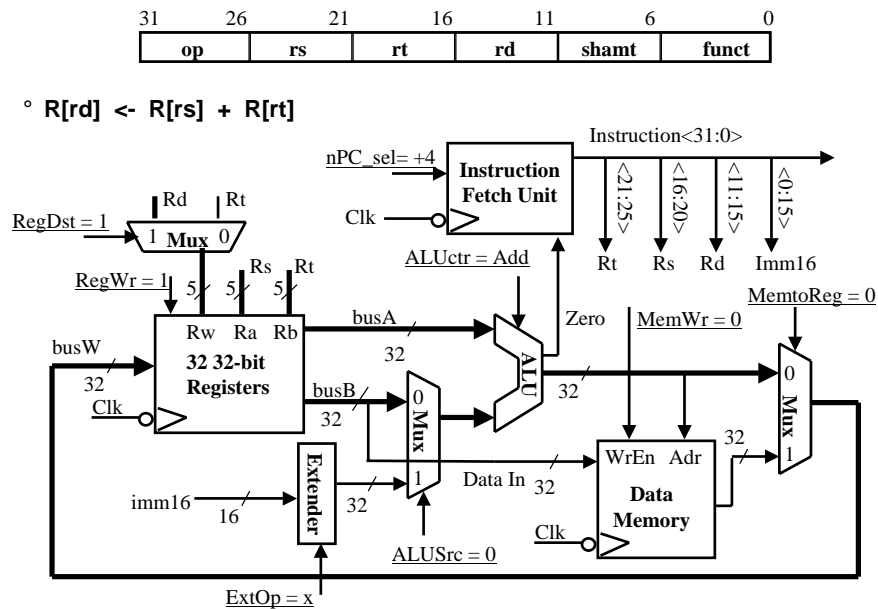


Instruction Fetch Unit at the End of Add

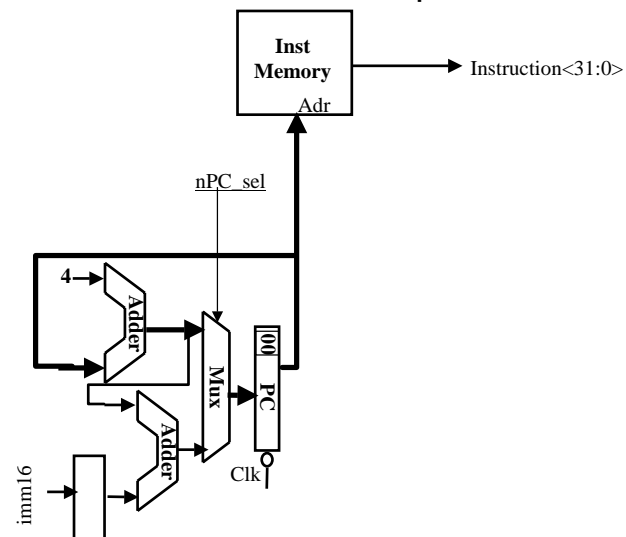
- $\text{PC} \leftarrow \text{PC} + 4$
 - This is the same for all instructions except: Branch and Jump



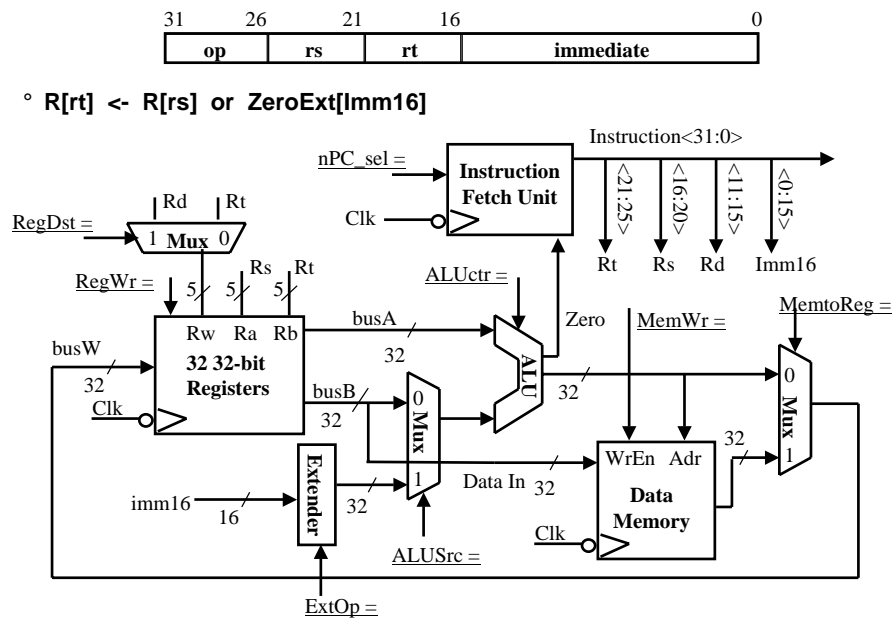
The Single Cycle Datapath during Or Immediate



 
The Single Cycle Datapath during Or Immediate



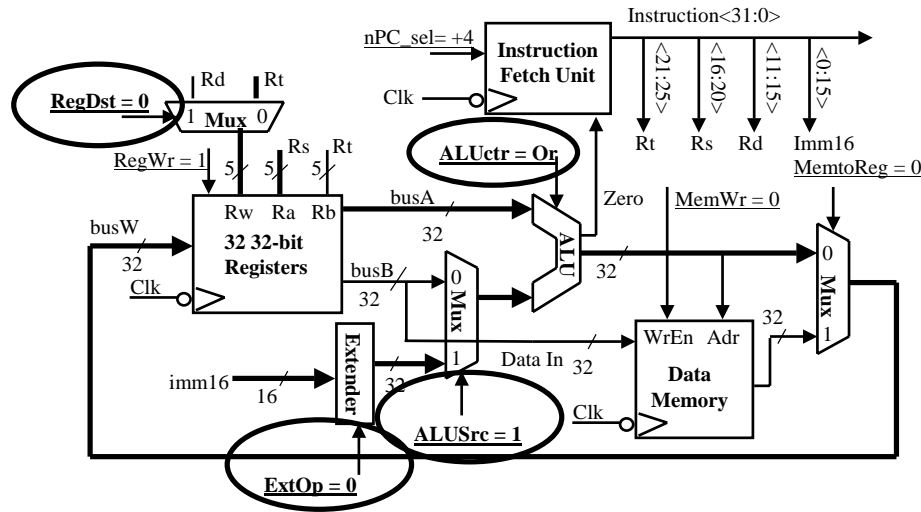
° $R[rt] \leftarrow R[rs] \text{ or } \text{ZeroExt}[\text{Imm16}]$




The Single Cycle Datapath during Load

 

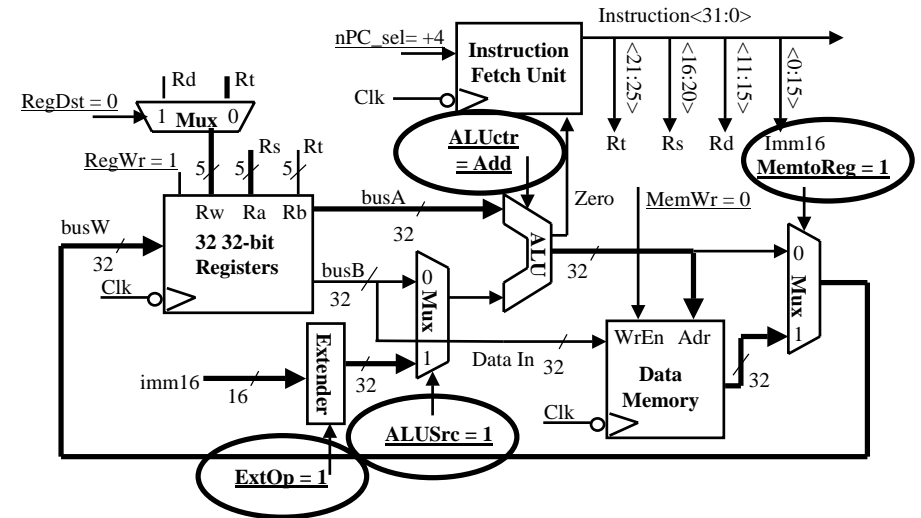
° $R[rt] \leftarrow \text{Data Memory } \{R[rs] + \text{SignExt}[\text{Imm16}]\}$




The Single Cycle Datapath during Store

 

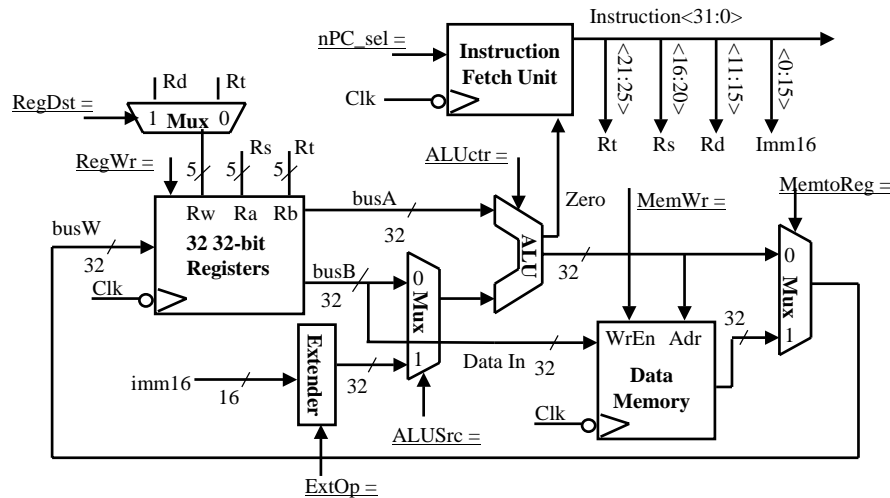
° $\text{Data Memory } \{R[rs] + \text{SignExt}[\text{Imm16}]\} \leftarrow R[rt]$




The Single Cycle Datapath during Store

 

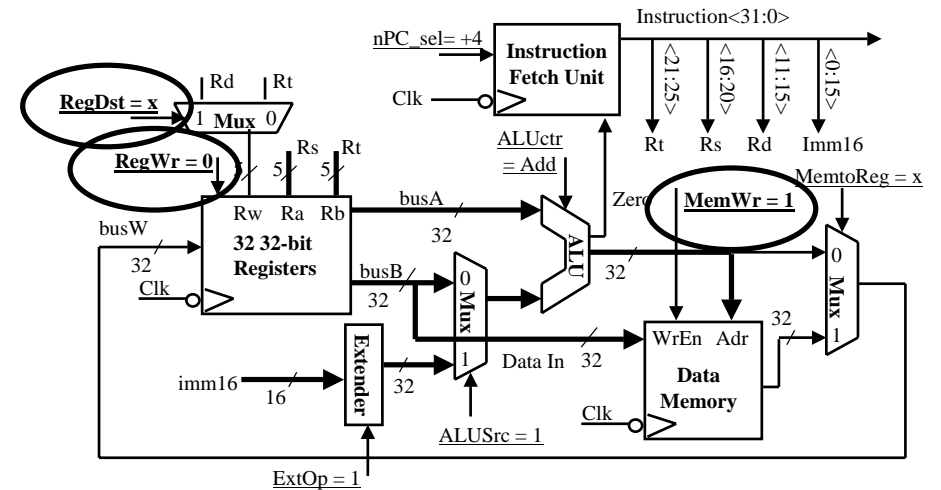
° $\text{Data Memory } \{R[rs] + \text{SignExt}[\text{Imm16}]\} \leftarrow R[rt]$




The Single Cycle Datapath during Branch

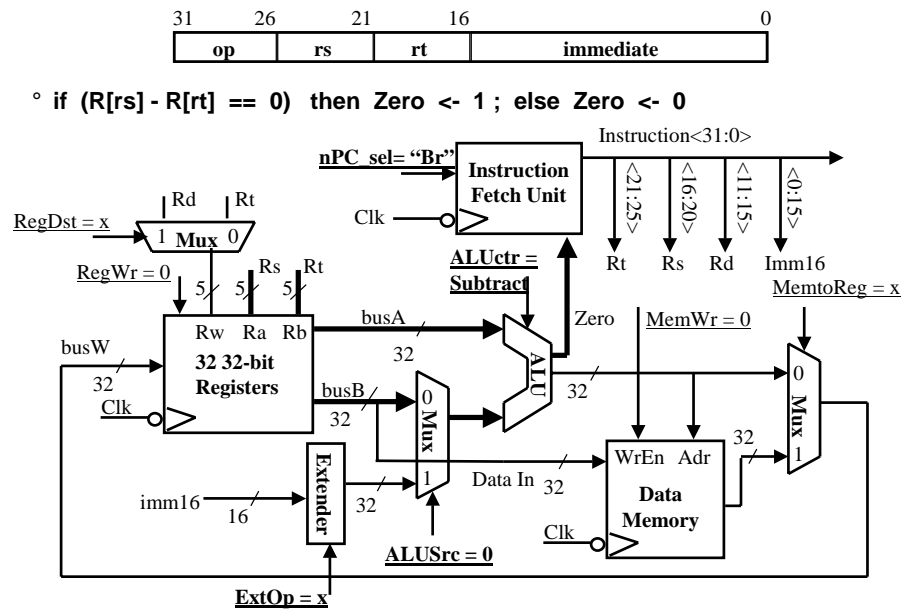

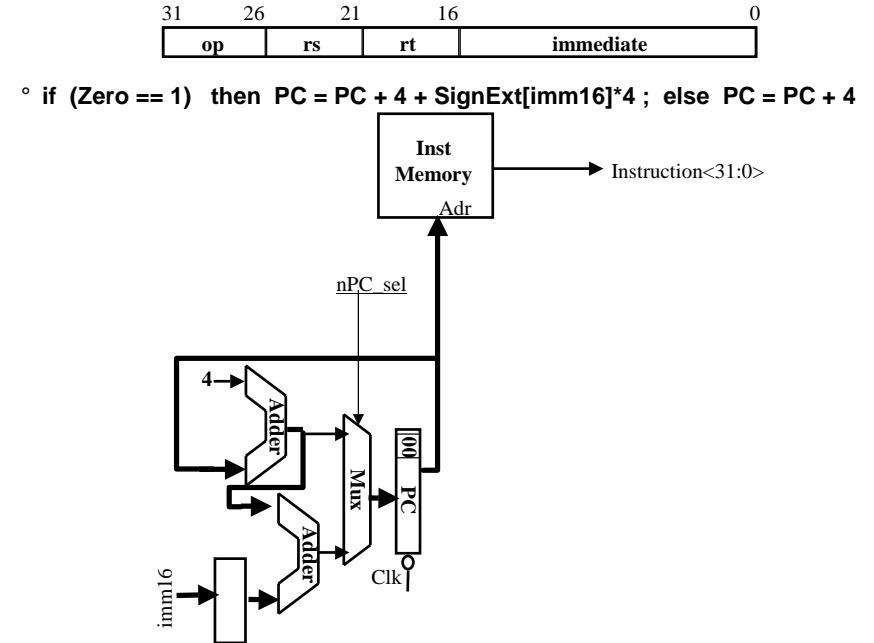Instruction Fetch Unit at the End of Branch



Step 4: Given Datapath: RTL -> Control

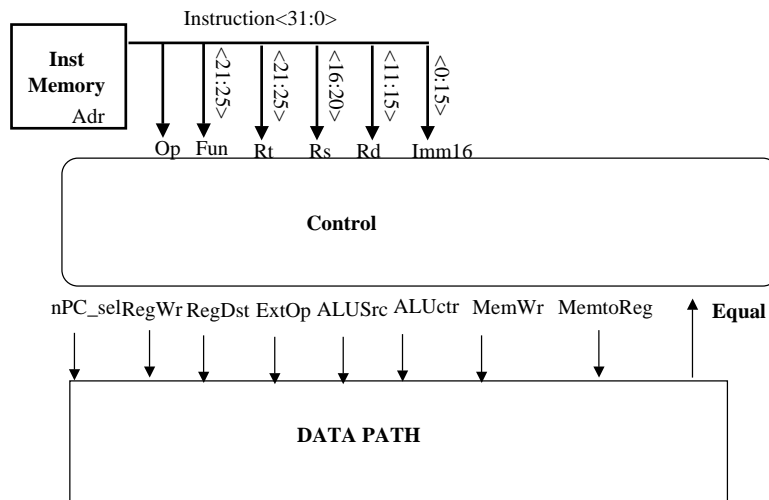

A Summary of Control Signals

<u>inst</u> <u>Register Transfer</u>		
ADD	$R[rd] \leftarrow R[rs] + R[rt];$ $ALUsrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"$	$PC \leftarrow PC + 4$
SUB	$R[rd] \leftarrow R[rs] - R[rt];$ $ALUsrc = RegB, ALUctr = "sub", RegDst = rd, RegWr, nPC_sel = "+4"$	$PC \leftarrow PC + 4$
ORI	$R[rt] \leftarrow R[rs] + zero_ext(Imm16);$ $ALUsrc = Im, Extop = "Z", ALUctr = "or", RegDst = rt, RegWr, nPC_sel = "+4"$	$PC \leftarrow PC + 4$
LOAD	$R[rt] \leftarrow MEM[R[rs] + sign_ext(Imm16)];$ $ALUsrc = Im, Extop = "Sn", ALUctr = "add",$ $MemtoReg, RegDst = rt, RegWr,$	$PC \leftarrow PC + 4$ $nPC_sel = "+4"$
STORE	$MEM[R[rs] + sign_ext(Imm16)] \leftarrow R[rs];$ $ALUsrc = Im, Extop = "Sn", ALUctr = "add", MemWr, nPC_sel = "+4"$	$PC \leftarrow PC + 4$
BEQ	if ($R[rs] == R[rt]$) then $PC \leftarrow PC + sign_ext(Imm16)$ 00 else $PC \leftarrow PC + 4$ $nPC_sel = "Br", ALUctr = "sub"$	

A Summary of the Control Signals


Predefined Codes (see Appendix A)

	func	10 0000	10 0010	We Don't Care :-)				
	op	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
		add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x	
ALUSrc	0	0	1	1	1	0	x	
MemtoReg	0	0	0	1	x	x	x	
RegWrite	1	1	1	1	0	0	0	
MemWrite	0	0	0	0	1	0	0	
nPCsel	0	0	0	0	0	1	0	
Jump	0	0	0	0	0	0	1	
ExtOp	x	x	0	1	1	x	x	
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	xxx	


	31	26	21	16	11	6	0	
R-type	op	rs	rt	rd	shamt	funct		add, sub
I-type	op	rs	rt	immediate				ori, lw, sw, beq
J-type	op	target address						jump

Local Decoding of ALU control signal

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUOp<N:0>	"R-type"	Or	Add	Add	Subtract	xxx

 

The Encoding of ALUOp

 

° For the MIPS subset we consider here, ALUOp has to be 2 bits wide to represent:


- (1) "R-type" instructions
- "I-type" instructions that require the ALU to perform:
 - (2) Or, (3) Add, and (4) Subtract

° To implement the full MIPS ISA, ALUOp has to be 3 bits to represent:

- (1) "R-type" instructions
- "I-type" instructions that require the ALU to perform:
 - (2) Or, (3) Add, (4) Subtract, and (5) And (Example: andi)

	R-type	ori	lw	sw	beq	jump
ALUOp (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUOp<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

The Decoding of the "func" Field

 


	R-type	ori	lw	sw	beq	jump
ALUOp (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUOp<2:0>	1 00	0 10	0 00	0 00	0 01	xxx

	31	26	21	16	11	6	0
R-type	op	rs	rt	rd	shamt	funct	

ALU control as defined in Ch 4

func<5:0>	Instruction Operation
10 0000	add
10 0010	subtract
10 0100	and
10 0101	or
10 1010	set-on-less-than

 

ALUctr<2:0>	ALU Operation
000	And
001	Or
010	Add
110	Subtract
111	Set-on-less-than

The Truth Table for ALUctr

ALUop (Symbolic)	R-type	ori	lw	sw	beq
ALUop<2:0>	“R-type”	Or	Add	Add	Subtract
ALUop<2:0>	1 00	0 10	0 00	0 00	0 01

funct<3:0>	Instruction Op.
0000	add
0010	subtract
0100	and
0101	or
1010	set-on-less-than

ALUop			func				ALU Operation	ALUctr		
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>		bit<2>	bit<1>	bit<0>
0	0	0	x	x	x	x	Add	0	1	0
0	x	1	x	x	x	x	Subtract	1	1	0
0	1	x	x	x	x	x	Or	0	0	1
1	x	x	0	0	0	0	Add	0	1	0
1	x	x	0	0	1	0	Subtract	1	1	0
1	x	x	0	1	0	0	And	0	0	0
1	x	x	0	1	0	1	Or	0	0	1
1	x	x	1	0	1	0	Set on <	1	1	1

The Logic Equation for ALUctr<2>

ALUop			func				ALUctr<2>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	x	1	x	x	x	x	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1

This makes func<3> a don't care

$$\circ \text{ALUctr<2>} = \text{!ALUop<2>} \& \text{ALUop<0>} + \text{ALUop<2>} \& \text{!func<2>} \& \text{func<1>} \& \text{!func<0>}$$

The Logic Equation for ALUctr<1>

ALUop			func				ALUctr<1>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	0	0	x	x	x	x	1
0	x	1	x	x	x	x	1
1	x	x	0	0	0	0	1
1	x	x	0	0	1	0	1
1	x	x	1	0	1	0	1


$$\circ \text{ALUctr<1>} = \text{!ALUop<2>} \& \text{!ALUop<0>} + \text{ALUop<2>} \& \text{!func<2>} \& \text{!func<0>}$$

The Logic Equation for ALUctr<0>

ALUop			func				ALUctr<0>
bit<2>	bit<1>	bit<0>	bit<3>	bit<2>	bit<1>	bit<0>	
0	1	x	x	x	x	x	1
1	x	x	0	1	0	1	1
1	x	x	1	0	1	0	1

$$\circ \text{ALUctr<0>} = \text{!ALUop<2>} \& \text{ALUop<0>} + \text{ALUop<2>} \& \text{!func<3>} \& \text{func<2>} \& \text{!func<1>} \& \text{func<0>} + \text{ALUop<2>} \& \text{func<3>} \& \text{!func<2>} \& \text{func<1>} \& \text{!func<0>}$$

The ALU Control Block

 

- $ALUctr<2> = !ALUop<2> \& ALUop<0> + ALUop<2> \& !func<2> \& func<1> \& !func<0>$
- $ALUctr<1> = !ALUop<2> \& !ALUop<0> + ALUop<2> \& !func<2> \& !func<0>$
- $ALUctr<0> = !ALUop<2> \& ALUop<0> + ALUop<2> \& !func<3> \& func<2> \& !func<1> \& func<0> + ALUop<2> \& func<3> \& !func<2> \& func<1> \& !func<0>$


Step 5: Logic for each control signal

- $nPC_sel \leq \text{if } (OP == BEQ) \text{ then } EQUAL \text{ else } 0$
- $ALUsrc \leq \text{if } (OP == \text{"Rtype"}) \text{ then "regB" else "immed"}$
- $ALUctr \leq \text{if } (OP == \text{"Rtype"}) \text{ then } funct \text{ elseif } (OP == ORI) \text{ then "OR" elseif } (OP == BEQ) \text{ then "sub" else "add"}$
- $ExtOp \leq \underline{\hspace{2cm}}$
- $MemWr \leq \underline{\hspace{2cm}}$
- $MemtoReg \leq \underline{\hspace{2cm}}$
- $RegWr: \leq \underline{\hspace{2cm}}$
- $RegDst: \leq \underline{\hspace{2cm}}$

Step 5: Logic for each control signal

- $nPC_sel \leq \text{if } (OP == BEQ) \text{ then } EQUAL \text{ else } 0$
- $ALUsrc \leq \text{if } (OP == \text{"Rtype"}) \text{ then "regB" else "immed"}$
- $ALUctr \leq \text{if } (OP == \text{"Rtype"}) \text{ then } funct \text{ elseif } (OP == ORI) \text{ then "OR" elseif } (OP == BEQ) \text{ then "sub" else "add"}$
- $ExtOp \leq \text{if } (OP == ORI) \text{ then "zero" else "sign"}$
- $MemWr \leq (OP == Store)$
- $MemtoReg \leq (OP == Load)$
- $RegWr: \leq \text{if } ((OP == Store) \parallel (OP == BEQ)) \text{ then } 0 \text{ else } 1$
- $RegDst: \leq \text{if } ((OP == Load) \parallel (OP == ORI)) \text{ then } 0 \text{ else } 1$

The "Truth Table" for the Main Control

 

op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegDst	1	0	0	x	x	x
ALUSrc	0	1	1	1	0	x
MemtoReg	0	0	1	x	x	x
RegWrite	1	1	1	0	0	0
MemWrite	0	0	0	1	0	0
Branch	0	0	0	0	1	0
Jump	0	0	0	0	0	1
ExtOp	x	0	1	1	x	x
ALUop (Symbolic)	"R-type"	Or	Add	Add	Subtract	xxx
ALUop <2>	1	0	0	0	0	x
ALUop <1>	0	1	0	0	0	x
ALUop <0>	0	0	0	0	1	x

The “Truth Table” for RegWrite


op	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	R-type	ori	lw	sw	beq	jump
RegWrite	1	1	1	0	0	0

° RegWrite = R-type + ori + lw


= !op<5> & !op<4> & !op<3> & !op<2> & !op<1> & !op<0> (R-type)

+ !op<5> & !op<4> & op<3> & op<2> & !op<1> & op<0> (ori)

 
+ op<5> & !op<4> & !op<3> & !op<2> & op<1> & op<0> (lw)




PLA Implementation of the Main Control

 

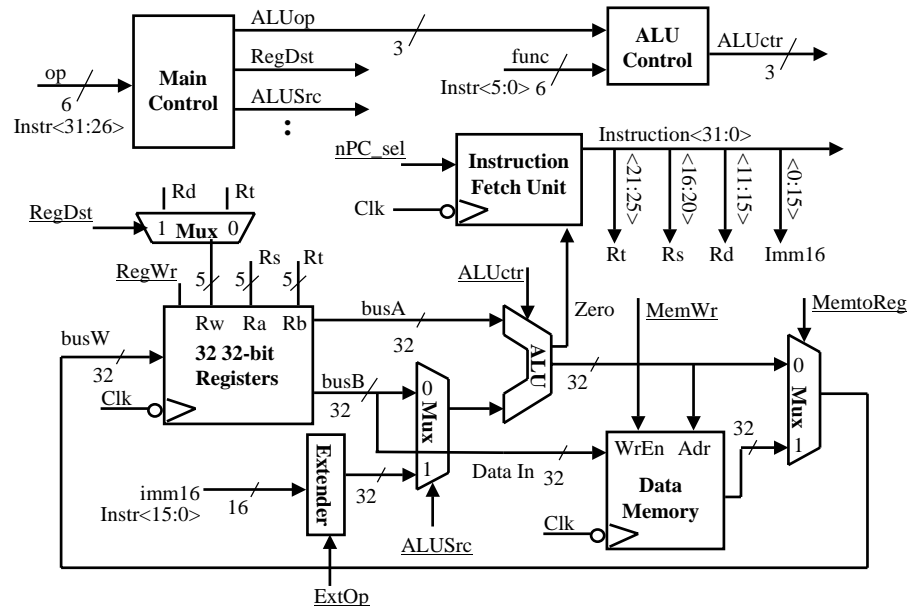Putting it All Together: A Single Cycle Processor



Worst Case Timing (Load)

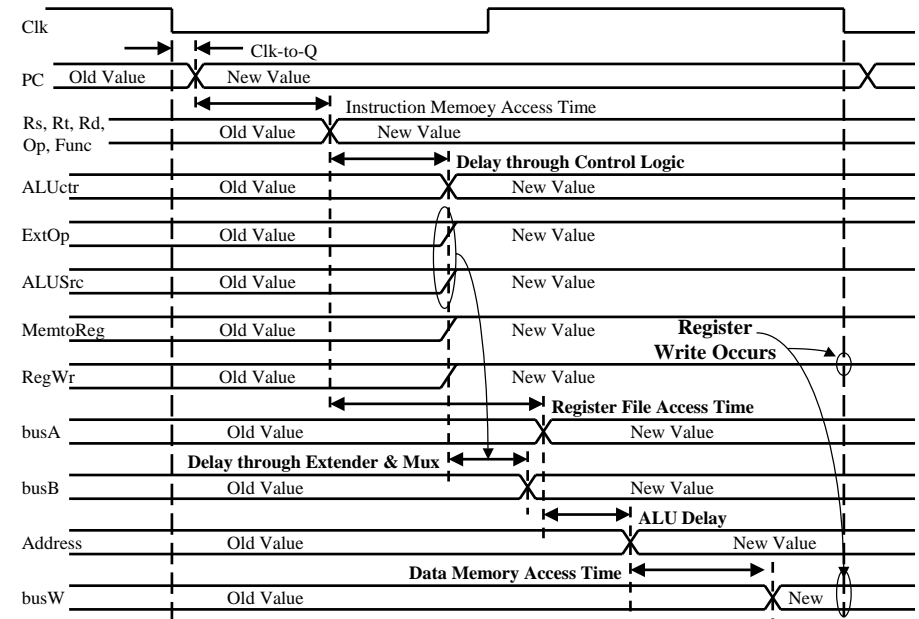

Drawback of this Single Cycle Processor

- Long cycle time:
 - Cycle time must be long enough for the load instruction:
PC's Clock -to-Q +
Instruction Memory Access Time +
Register File Access Time +
ALU Delay (address calculation) +
Data Memory Access Time +
Register File Setup Time +
Clock Skew
- Cycle time for load is much longer than needed for all other instructions

Summary

- Single cycle datapath => CPI=1, CCT => long


- 5 steps to design a processor

- 1. Analyze instruction set => datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic

- Control is the hard part

- MIPS makes control easier

 - Instructions same size
- Source registers always in same place
- Immediates same size, location
- Operations always on registers/immediates



Where to get more information?

- Chapter 5.1 to 5.3 of the text:
 - David Patterson and John Hennessy, "Computer Organization & Design: The Hardware / Software Interface," Second Edition, Morgan Kaufman Publishers, San Mateo, California, 1998.
- A good PhD thesis on processor design:
 - Manolis Katevenis, "Reduced Instruction Set Computer Architecture for VLSI," PhD Dissertation, EECS, U C Berkeley, 1982.
- For a reference on the MIPS architecture:
 - Gerry Kane, "MIPS RISC Architecture," Prentice Hall.