

L3: Background Part 3 – VHDL

Notices & reminders

- Lecture time for Friday 29/08: 9:00 – 11:00
- I will only respond to email that requires administrative involvement by the LiC, or that raises a query about coursework that a tutor has not been able to answer
 - Email martindg@cse for web related, administrative, or organisational matters
 - Email your_tutor@cse for queries about coursework, and CC: to comp3211_tutor-list@cse
 - Send from a UNSW mail service

COMP3211/9211

2003 S2 L3 P2

Overview

This lecture

1. Introduction to VHDL
 - Use in describing systems
2. Describing & modelling systems
 - Signals, events, timing, concurrency
 - Use of discrete event simulation

Next few lectures

3. Basic language constructs
 - Describing the interface and behaviour of components
 - Signal assignments
 - Delays
 - Modelling complex behaviour
 - Modelling state machines
 - Modelling structure
 - Subprograms, packages, and libraries

COMP3211/9211

2003 S2 L3 P2


1. Introduction to VHDL

- Use in describing systems

COMP3211/9211


2003 S2 L3 P3

Describing Digital Systems

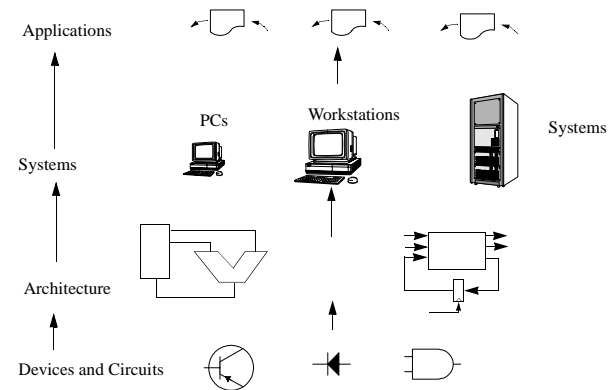

- Systems may be described at multiple levels of abstraction


The Digital System Design Process

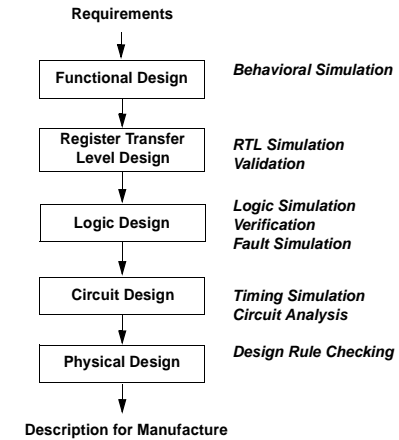

Why Do We Describe Systems?

- Design Specification
 - unambiguous definition of components and interfaces in a large design
- Design Simulation
 - verify system/subsystem/chip performance prior to design implementation
- Design Synthesis
 - automated generation of a hardware design

Hardware Description Languages

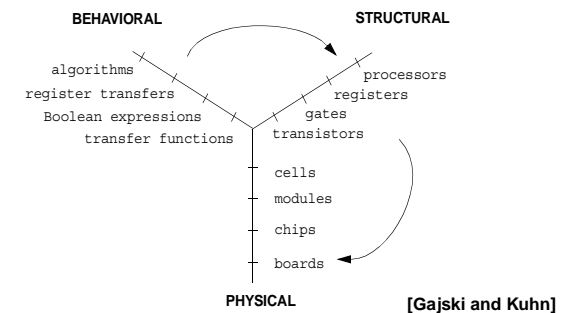

- Design is structured around a hierarchy of representations
- HDLs can describe distinct aspects of a design at multiple levels of abstraction

The VHDL Language

V *Very High Speed Integrated Circuit*

H *Hardware*

D *Description*

L *Language*

- Interoperability between design tools: standardized portable model of electronic systems
- Technology independent description
- Reuse of components described in VHDL


History of VHDL

- Designed by IBM, Texas Instruments, and Intermetrics as part of the DoD funded VHSIC program
- Standardized by the IEEE in 1987: IEEE 1076-1987
- Enhanced version of the language defined in 1993: IEEE 1076-1993
- Additional standardized packages provide definitions of data types and expressions of timing data
 - IEEE 1164 (data types)
 - IEEE 1076.3 (numeric)
 - IEEE 1076.4 (timing)

2. Describing & modelling systems


- Signals, events, timing, concurrency
- Use of discrete event simulation

Describing Systems

 


- System: "An assemblage of objects united by some form or regular interaction or dependence"
- What aspects of a digital system do we want to describe?
 - interface
 - behavior: functional and structural

Behavioral Attributes of Digital Systems

 


- Digital systems are about *signals* and their *values*
- *Events*, *propagation delays*, *concurrency*
- Time ordered sequence of events produces a *waveform*

Behavioral Attributes of Digital Systems

 


- *Timing*: computation of events takes place at specific points in time
- Timing is an attribute of both synchronous and asynchronous systems

Simulation of Digital Systems

 


- Digital systems propagate events
- Discrete event simulations manage the generation and recording of events

Simulation Modeling

 


- VHDL programs describe the generation of events in digital systems
- Discrete event simulator manages event ordering and progression of time

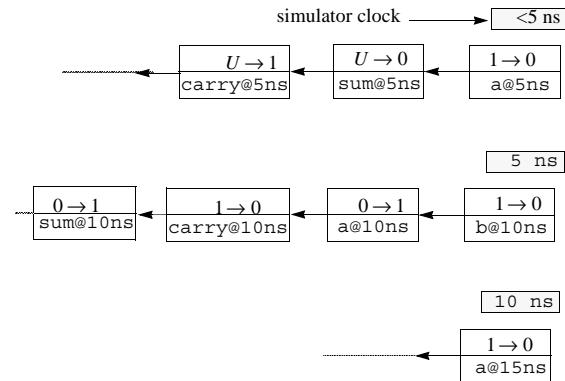Discrete Event Simulation: Half Adder Model



- Management of simulation time: ordering of events
- Two step model of the progression of time

Behavioral Attributes of Digital Systems

 

- Digital systems are about *signals* and their *values*
- *Events*, *propagation delays*, *concurrency*
- Time ordered sequence of events produces a *waveform*


Modeling Digital Systems

- VHDL programs describe behavioral attributes of digital systems
 - events, propagation delays, concurrency
 - waveforms and timing
 - signal values
- Discrete event simulators mimic the operation of the system being described
 - two step model of time
 - assign values scheduled for signals at the current time
 - process affected components and schedule future signal values
 - ensures events are generated and processed in the correct order
 - a correct simulation generates *only and all* those events that would have been generated in the physical system

3. Basic language constructs


- Describing the interface and behaviour of components
- Signal assignments
- Delays
- Modelling complex behaviour
- Modelling state machines
- Modelling structure
- Subprograms, packages, and libraries

Basic Language Concepts

 

- What aspects of a digital system do we want to describe?
 - interface: how do we connect to it
 - behavior: what does it do?

 
Describing the Interface: The Entity Construct




```
entity half_adder is
  port ( a, b : in bit;
         sum, carry : out bit);
end half_adder;
```

- The interface is a collection of *ports*
 - ports are a new programming object: *signal*
 - ports have a type, e.g., **bit**
 - ports have a mode: in, out, inout (bidirectional)

Example Entity Descriptions

 

 
```
entity ALU32 is
  port( A, B : in bit_vector (31 downto 0);
        C : out bit_vector (31 downto 0);
        Op : in bit_vector (5 downto 0);
        N, Z : out bit);
end ALU32;
```



```
entity D_ff is
  port( D, Q, Clk, R, S : in bit;
        Q, Qbar : out bit);
end D_ff;
```

 Describing Behavior: The Architecture Construct




```
entity half_adder is
  port (a, b : in bit;
        sum, carry : out bit);
end half_adder;

architecture behavioral of half_adder
  is
  begin
    sum <= (a xor b) after 5 ns;
    carry <= (a and b) after 5 ns;
  end behavior;
```

- Description of events on output signals in terms of events on input signals: the *signal assignment statement*
- Specification of propagation delays
- Type **bit** is not powerful enough for realistic simulation: use the IEEE 1164 value system

Behavioral Attributes of Digital Systems

 
- We associate logical values with the state of a signal




- Signal Values: IEEE 1164 Value System

Value	Interpretation
U	Uninitialized
X	Forcing Unknown
0	Forcing 0
1	Forcing 1
Z	High Impedance
W	Weak Unknown
L	Weak 0
H	Weak 1
-	Don't Care

Example Entity Descriptions: IEEE 1164

 

 
```
entity ALU32 is
port( A,B: in std_logic_vector (31 downto 0);
      C: out std_logic_vector (31 downto 0);
      Op: in std_logic_vector (5 downto 0);
      N,Z: out std_logic);
end ALU32;
```



```
entity D_ff is
port( D,Q,Clk,R,S: in std_ulogic;
      Q,Qbar: out std_ulogic);
end D_ff;
```

 Describing Behavior: The Architecture Construct




```
library IEEE;
use IEEE.std_logic_1164.all;

entity half_adder is
port ( a,b : in std_logic;
       sum, carry : out std_logic);
end half_adder;
```

```
architecture behavioral of half_adder
is
begin
sum <= (a xor b) after 5 ns;
carry <= (a and b) after 5 ns;
end behavior;
```

- Use of the IEEE 1164 value system simply requires inclusion of the library and package declarations statements

Design Units

 

- An entity may have multiple architectures
- Separation of interface from implementation


Simple Signal Assignment

```

library IEEE;
use IEEE.std_logic_1164.all;
entity full_adder is
port (in1, in2, c_in: in std_logic;
      sum, c_out: out std_logic);
end full_adder;

architecture dataflow of full_adder is
signal s1, s2, s3 : std_logic;
constant gate_delay: Time:= 5 ns;
begin
L1: s1 <= (In1 xor In2) after gate_delay;
L2: s2 <= (c_in and s1) after gate_delay;
L3: s3 <= (In1 and In2) after gate_delay;
L4: sum <= (s1 xor c_in) after gate_delay;
L5: c_out <= (s2 or s3) after gate_delay;
end dataflow;


```

 

Simple Signal Assignment Statement

- The *constant* programming object
 - values cannot be changed
- Use of signals in the architecture
 - internal signals used to connect components
- A statement is executed when a signal in the RHS has value assigned to it
 - 1-1 correspondence between signal assignment statements and signals in the circuit
 - order of statement execution follows propagation of events in the circuit
 - textual order *does not* imply execution order
 - trace the statement execution order when In1 changes value

Understanding Delays

 


- Inertial delay model
- Transport delay model
- Delta delay model

Understanding Delays

- Inertial delay
 - default delay model
 - suitable for modeling delays through devices such as gates
- Transport Delay
 - to model delays through devices with very small inertia, e.g, wires
 - all input events are propagated to output signals
- Delta delay
 - what about models where no propagation delays are specified?
 - infinitesimally small delay is automatically inserted by the simulator to preserve correct ordering of events

Transport Delays: Example

 
```
architecture transport_delay of
half_adder is
signal s1,s2:std_logic:= '0';
begin
s1 <= (a xor b) after 2 ns;
s2 <= (a and b) after 2 ns;
sum <= transport s1 after 4 ns;
carry <= transport s2 after 4 ns;
end transport_delay;
```




Delta Delays: Example

```
library IEEE;
use IEEE.std_logic_1164.all;
entity combinational is
port (In1, In2: in std_logic;
      z : out std_logic);
end combinational;
```
 
```
architecture behavior of
combinational is
signal s1,s2,s3,s4:std_logic:=
begin
s1 <= not In1;
s2 <= not In2;
s3 <= not (s1 and In2);
s4 <= not (s2 and In1);
z <= not (s3 and s4);
end behavior;
```



Delta Delays: Example

 

Conditional Signal Assignment

```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
      Sel: in std_logic_vector (1 downto 0);
      Z : out std_logic_vector (7 downto 0));
end mux4;
```

```
architecture behavioral of mux4 is
begin
```

```
Z <= In0 after 5 ns when Sel = "00" else
      In1 after 5 ns when Sel = "01" else
      In2 after 5 ns when Sel = "10" else
      In3 after 5 ns when Sel = "11" else
      "00000000" after 5 ns;
```

```
end behavioral;
```

← Evaluation order
is important!

- First true conditional determines the output value

Selected Signal Assignment Statement


```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
      Sel: in std_logic_vector(1 downto 0);
      Z :out std_logic_vector (7 downto 0));
end mux4;

architecture behavioral-2 of mux4 is
begin
with Sel select
Z <= (In0 after 5 ns) when "00",
      (In1 after 5 ns) when "01",
      (In2 after 5 ns) when "10",
      (In3 after 5 ns) when "11"
      (In3 after 5 ns) when others;
end behavioral;
```

← All options must be covered and only one must be true!

- The “when others” clause can be used to ensure that all options are covered

Modeling Complex Behavior

 

```
add R1, R2, R3
sub R3, R4, R5
move R7, R3
```

Instruction Set Simulation

- Concurrent signal assignment statements can easily capture the gate level behavior of digital systems
- Higher level digital components have more complex behaviors
 - input/output behavior not easily captured by concurrent signal assignment statements
 - models utilize state information
 - incorporate data structures
- We need more powerful constructs

The Process Statement

```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
      Sel: in std_logic_vector(1 downto 0);
      Z :out std_logic_vector (7 downto 0));
end mux4;

architecture behavioral-3 of mux4 is
begin
process (Sel, In0, In1, In2, In3)
variable Zout: std_logic;
begin
  if (Sel = "00") then Zout:= In0;
  elsif (Sel = "01") then Zout:= In1;
  elsif (Sel = "10") then Zout:= In2;
  else Zout:= In3;
  end if;
  Z <= Zout;
end process;
end behavioral;
```


→ Sensitivity List

→ Variable Assignment

The Process Construct

- Statements in a process are executed sequentially
- A process body is structured much like conventional C or Pascal programs
 - declaration and use of variables
 - *if-then*, *if-then-else*, *case*, *loop* and *while* constructs
 - process can contain signal assignment statements
- A process executes concurrently with other concurrent signal assignment statements
- A process takes 0 simulation time to execute and may schedule events in the future: we can think of a process as a complex signal assignment statement!

Concurrent Processes: Full Adder

 

- Each of the components of the full adder can be modeled using a process
- Processes execute concurrently
- Processes communicate via signals

Concurrent Processes: Full Adder

```
library IEEE;
use IEEE.std_logic_1164.all;

entity full_adder is
    port (In1, c_in, In2 : in std_logic;
          sum, c_out : out std_logic);
end full_adder;

architecture behavioral of
    full_adder is
        signal s1, s2, s3 : std_logic;
        constant delay : Time := 5 ns;
    begin
        HA1: process (In1, In2)
        begin
            s1 <= (In1 xor In2) after delay;
            s3 <= (In1 and In2) after delay;
        end process HA1;

        HA2: process (s1, c_in)
        begin
            sum <= (s1 xor c_in) after
            delay;
            s2 <= (s1 and c_in) after delay;
        end process HA2;

        OR1: process (s2, s3) -- process
            describing the two-input OR gate
        begin
            c_out <= (s2 or s3) after delay;
        end process OR1;
    end behavioral;
```

Concurrent Processes: Half Adder

```
library IEEE;
use IEEE.std_logic_1164.all;

entity half_adder is
    port (a, b : in std_logic;
          sum, carry : out std_logic);
end half_adder;

architecture behavior of
    half_adder is
    begin
        sum_proc: process(a,b)
        begin
            if (a = b) then
                sum <= '0' after 5 ns;
            else
                sum <= (a or b) after 5 ns;
            end if;
        end process;

        carry_proc: process(a,b)
        begin
            case a is
                when '0' =>
                    carry <= a after 5 ns;
                when '1' =>
                    carry <= b after 5 ns;
                when others =>
                    carry <= 'X' after 5 ns;
            end case;
        end process carry_proc;
    end behavior;
```

The Wait Statement

```
library IEEE;
use IEEE.std_logic_1164.all;

entity dff is
    port (D, Clk : in std_logic;
          Q, Qbar : out std_logic);
end dff;

architecture behavioral of dff is
    begin
        output: process
        begin
            wait until (Clk'event and Clk = '1'); -- wait for edge

            Q <= D after 5 ns;
            Qbar <= not D after 5 ns;
        end process output;
    end behavioral;
```

signifies a value change on signal clk

- wait for <time expression>, wait on <signal>, wait until <boolean expression>

The Wait Statement: Waveform Generation

```

library IEEE;
use IEEE.std_logic_1164.all;
entity two_phase is
port (phi1, phi2, reset: out
std_logic);
end two_phase;


architecture behavioral of
two_phase is
begin
rproc: reset <= '1', '0' after 10 ns;

```

```

clock_process: process
begin
phi1 <= '1', '0' after 10 ns;
phi2 <= '0', '1' after 12 ns, '0' after
18 ns;
wait for 20 ns;
end process clock_process;
end behavioral;

```

 

The Wait Statement

- A process can have multiple wait statements
- A process cannot have both a wait statement and a sensitivity list (it should have one or the other)

VHDL Identifiers, Objects, Types, & Operators

- Identifiers
 - Used as names for variables, signals, constants, and design units such as entities, architectures, etc.
 - Composed of alphanumeric characters and underscore
 - Must start with a letter; may not end with underscore
 - Are not case-sensitive

Data Objects

- Classes: signals, variables, constants, and files
- Range of permissible values determined by type
 - Signals represent wires
 - Signals differ from variables in that:
 - Signals are scheduled to receive values at some time by the simulator, and one can schedule multiple values at distinct instants in the future
 - Variables are assigned during execution of assignment statements and can only be assigned one value at a time – variables are essentially equivalent to their conventional programming language counterparts
 - Constants must be declared & initialized at start of simulation & cannot be modified during the simulation

Data Types

- Specify the range of values an object may take and the set of operations that can be performed on it:

Type	Range of values	Example declaration
integer	implementation dependent	signal index: integer :=0;
real	implementation dependent	variable val: real :=1.0;
boolean	(TRUE,FALSE)	variable test: boolean :=TRUE;
character	defined in package STANDARD	variable term: character := '@';
bit	0, 1	signal ln1: bit :=0';
bit_vector	array of bit	variable PC: bit_vector (31 downto 0);
time	implementation dependent	variable delay: time :=25 ns;
string	array of char	variable name: string (1 to 10):="model name";
natural	0 to maxint	variable index: natural :=0;
positive	1 to maxint	variable index: positive :=1;

Enumerated Types

- The standard set provided by VHDL can be augmented through user-defined types
- Consider trouble with "bit" signals, thus we have:

```
type std_ulogic is ('U','0','1',  
                    'Z','W','L','H','-');
```

then we can declare

```
signal carry:std_ulogic:='U';
```

- The definition explicitly enumerates all possible values that an object of this type can assume

Another example

- Define new type:

```
type instr_opcode is  
    ('add','lw','beq',...);
```

then can have

```
case opcode  
when beq =>...
```

- Can place such type declarations in declarative region of architecture, process, or package

Array Types

- Very common in hardware, e.g., a word is an array of bits, memory an array of words, a data bus an array of data lines...
- E.g.

```
type byte is  
    array (7 downto 0) of bit;
```

Physical Types

- Motivated by need to represent physical quantities such as time, voltage, power, etc.
- E.g., **type** time **is range** 0 **to** 1000000

units

fs;

ps = 1000 fs;

ns = 1000 ps;...

hr = 60 min;

end units;

COMP3211/9211

2003 S2 L3 P13

Operators

- Used in expressions involving objects

logical operators	and	or	nand	nor	xor	xnor
relational operators	=	/=	<	<=	>	>=
shift operators	sll	srl	sla	sra	rol	ror
addition operators	+	-	&			
unary operators	+	-				
multiplying operators	*	/	mod	rem		
miscellaneous operators	**	abs	not			

- There is increasing precedence from top to bottom
- All operators within the same class have the same precedence and are evaluated in textual order from left to right
- Use parentheses to control evaluation order

COMP3211/9211


2003 S2 L3 P14

Attributes

- Data can be obtained about VHDL items such as types, arrays and signals.

object'**attribute**

 - Example: consider the implementation of a signal



- what types of information about this signal are useful?
 - occurrence of an event
 - elapsed time since last event
 - previous value

Value Kind Attributes

- Return a constant value

type statetype **is** (state0, state1, state2 state3);

- state_type'**left** = state0
- state_type'**right** = state3

Value attribute	Value
type_name' left	returns the left most value of type_name in its defined range
type_name' right	returns the right most value of type_name in its defined range
type_name' high	returns the highest value of type_name in its range
type_name' low	returns the lowest value of type_name in its range
array_name' length	returns the number of elements in the array array_name

Function Kind Attributes


- Use of attributes invokes a function call which returns a value
if (clk'event and clk = '1')

function call

- Function signal attributes

Function attribute	Function
signal_name'event	Return a Boolean value signifying a change in value on this signal
signal_name'active	Return a Boolean value signifying an assignment made to this signal. This assignment may not be a new value.
signal_name'last_event	Return the time since the last event on this signal
signal_name'last_active	Return the time since the signal was last active
signal_name'last_value	Return the previous value of this signal

State Machines

 

- Basic components
 - combinational component: output function and next state function
 - sequential component
- Natural process implementation

Example: State Machine

```

library IEEE;
use IEEE.std_logic_1164.all;
entity state_machine is
port(reset, clk, x : in std_logic;
      z : out std_logic);
end state_machine;

architecture behavioral of state_machine is
type statetype is (state0, state1);
signal state, next_state : statetype := state0;
begin
  comb_process: process(state, x)
  begin
    --- process description here
  end process comb_process;

  clk_process: process
  begin
    -- process description here
  end process clk_process;
end behavioral;

```

Example: Output and Next State Functions

```

comb_process: process(state, x)
begin
  case state is -- depending upon the current state
    when state0 => -- set output signals and next state
      if x = '0' then
        next_state <= state1;
        z <= '1';
      else next_state <= state0;
        z <= '0';
      end if;
    when state1 =>
      if x = '1' then
        next_state <= state0;
        z <= '0';
      else next_state <= state1;
        z <= '1';
      end if;
  end case;
end process comb_process;

```

- Combination of the next state and output functions

Example: Clock Process


```

clk_process: process
begin
wait until (clk'event and clk = '1'); -- wait until the rising edge
if reset = '1' then -- check for reset and initialize state
state <= statetype'left;
else state <= next_state;
end if;
end process clk_process;
end behavioral;

```


- Use of asynchronous reset to initialize into a known state

Modeling Structure

 

- Structural models describe a digital system as an interconnection of components
- Descriptions of the components must be available as structural or behavioral models

Modeling Structure

 

- Define the components used in the design
- Describe the interconnection of these components

Modeling Structure

```

architecture structural of full_adder is
component half_adder -- the declaration
port (a,b: in std_logic; -- of components you will use
      sum,carry: out std_logic);
end component;

component or_2
port (a,b: in std_logic;
      c: out std_logic);
end component;

signal s1,s2,s3: std_logic;
begin
H1: half_adder port map (a => In1, b => In2, sum=>s1, carry=>s3);
H2: half_adder port map (a => s1, b => c_in, sum=>sum,
                        carry => s2);
O1: or_2 port map (a => s2, b => s3, c => c_out);
end structural;

```

Annotations for the code:

- unique name of the components: `half_adder`, `or_2`
- component type: `half_adder`, `or_2`
- interconnection of the component ports: `port map` statements
- component instantiation statement: `H1:`, `H2:`, `O1:`


- Entity/architecture for half_adder and or_2 must exist

Hierarchy and Abstraction

```
architecture structural of half_adder is
  component xor2
    port (a,b : in std_logic;
          c : out std_logic);
  end component;
  component and2
    port (a,b : in std_logic;
          c : out std_logic);
  end component;
begin
  EX1: xor2 port map (a => a, b => b, c => sum);
  AND1: and2 port map (a => a, b => b, c => carry);
end structural;
```

- Structural descriptions can be nested
- The half adder may itself be a structural model

Hierarchy and Abstraction

 

- Nested structural descriptions to produce hierarchical models
- The hierarchy is flattened prior to simulation
- Behavioral models of components at the bottom level must exist

Generics

```
library IEEE;
use IEEE.std_logic_1164.all;

entity xor2 is
  generic (gate_delay: Time := 2 ns);
  port (In1, In2 : in std_logic;
        z : out std_logic);
end xor2;

architecture behavioral of xor2 is
begin
  z <= (In1 xor In2) after gate_delay;
end behavioral;
```

- Enables the construction of parameterized models

Generics in Hierarchical Models


```
architecture generic_delay of half_adder is
  component xor2
    generic (gate_delay: Time);
    port (a,b : in std_logic;
          c : out std_logic);
  end component;

  component and2
    generic (gate_delay: Time);
    port (a,b : in std_logic;
          c : out std_logic);
  end component;


begin
  EX1: xor2 generic map (gate_delay => 6 ns)
    port map (a => a, b => b, c => sum);
  A1: and2 generic map (gate_delay => 3 ns)
    port map (a => a, b => b, c => carry);
end generic_delay;
```

- Parameter values are passed through the hierarchy

Example: Full Adder

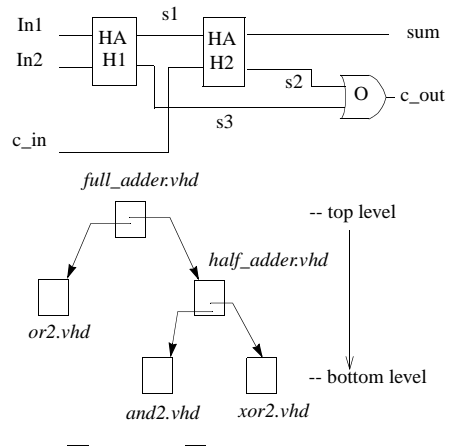

Example: Full Adder

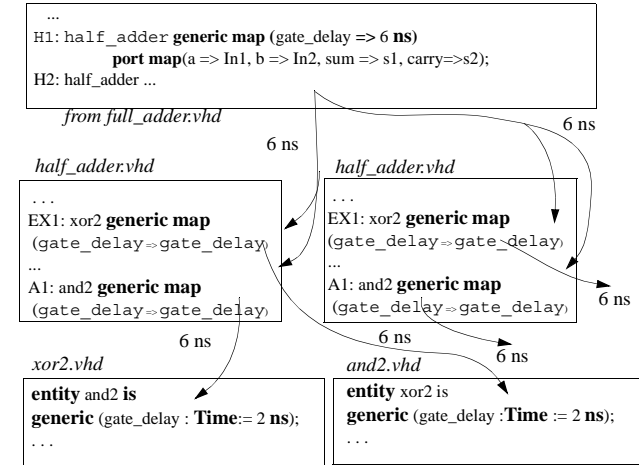

Precedence of Generic Declarations

```
architecture generic_delay2 of half_adder is
  component xor2
    generic (gate_delay: Time);
    port (a, b : in std_logic;
          c : out std_logic);
  end component;
```

```
  component and2
    generic (gate_delay: Time:= 6 ns);
    port (a, b : in std_logic;
          c : out std_logic);
  end component;
```

```
  begin
    EX1: xor2 generic map (gate_delay => gate_delay)
      port map(a => a, b => b, c => sum);
    A1: and2 generic map (gate_delay => 4 ns)
      port map(a=> a, b=> b, c=> carry);
  end generic_delay2;
```

takes precedence

- Generic map takes precedence over the component declaration

Example: N-Input Gate

```
entity generic_or is
  generic (n: positive:=2);
  port (in1 : in std_logic_vector((n-1) downto 0);
        z : out std_logic);
end generic_or;
```

```
architecture behavioral of generic_or is
  begin
    process (in1)
      variable sum: std_logic:= '0';
    begin
      sum := '0'; -- on an input signal transition sum must be reset t
      for i in 0 to (n-1) loop
        sum := sum or in1(i);
      end loop;
      z <= sum;
    end process;
  end behavioral;
```

- Map the generics to create different size OR gates

Example: Using the Generic N-Input OR Gate

```

architecture structural of full_adder is
component generic_or
generic (n: positive);
port (in1 : in std_logic_vector ((n-1) downto 0);
      z : out std_logic);
end component;
...
-- remainder of the declarative region from earlier example
...
begin
H1: half_adder port map (a => In1, b => In2, sum=>s1, carry=>s3);
H2: half_adder port map (a => s1, b => c_in, sum=>sum,
                        carry => s2);
O1: generic_or generic map (n => 2)
    port map (a => s2, b => s3, c => c_out);
end structural;

```

- Full adder model can be modified to use the generic OR gate model via the **generic map ()** construct

Example: N-bit Register

```


entity generic_reg is
generic (n: positive:=2);
port (clk, reset, enable : in std_logic;
      d : in std_logic_vector (n-1 downto 0);
      q : out std_logic_vector (n-1 downto 0));
end generic_reg;

architecture behavioral of generic_reg is
begin
reg_process: process (clk, reset)
begin
if reset = '1' then
q <= (others => '0');
elsif (clk'event and clk = '1') then
if enable = '1' then q <= d;
end if;
end if;
end process reg_process;
end behavioral;

```


- This model is used in the same manner as the generic OR gate

Configurations

 

- A design entity can have multiple alternative architectures
- A configuration specifies the architecture that is to be used to simulate a design entity

Component Binding

 

- Concerned with configuring the architecture and not the entity
- Enhances sharing of designs: simply change the configuration

Default Binding Rules

```
architecture structural of serial_adder is
component comb
port (a, b, c_in : in std_logic;
      z, carry : out std_logic);
end component;

component dff
port (clk, reset, d :in std_logic;
      q, qbar :out std_logic);
end component;

signal s1, s2 : std_logic;
begin
C1: comb port map (a => a, b => b, c_in => s1, z => z, carry => s2);
D1: dff port map (clk => clk, reset => reset, d => s2, q => s1, qbar => open);
end structural;
```

- Search for entity with the same component name
- Bind the last compiled architecture for that entity
- How do we get more control over binding?

Configuration Specification

```
architecture structural of full_adder is
--
--declare components here
signal s1, s2, s3: std_logic;
--
-- configuration specification
for H1: half_adder use entity WORK.half_adder (behavioral);
for H2: half_adder use entity WORK.half_adder (structural);
for O1: or_2 use entity POWER.lpo2 (behavioral)
generic map (gate_delay => gate_delay)
port map (I1 => a, I2 => b, Z => c);

begin
-- component instantiation statements
H1: half_adder port map (a => In1, b => In2,
                        sum => s1, carry => s2);
H2: half_adder port map (a => s1, b => c_in,
                        sum => sum, carry => s2);
O1: or_2 port map (a => s2, b => s3, c => c_out);
end structural;
```

- We can specify any binding where ports and arguments match

Configuration Declaration

```
configuration Config_A of full_adder is -- name the configuration
-- for the entity
for structural -- name of the architecture being configured
for H1: half_adder use entity WORK.half_adder (behavioral);
end for;
--
for H2: half_adder use entity WORK.half_adder (structural);
end for;
--
for O1: or_2 use entity POWER.lpo2 (behavioral)
generic map (gate_delay => gate_delay)
port map (I1 => a, I2 => b, Z => c);
end for;
--
end for;
end Config_A;
```


- Separate design unit
- Can be written to span a design hierarchy

Essentials of Functions

```
function rising_edge (signal clock: std_logic) return boolean is
--
--declarative region: declare variables local to the function
--
begin
-- body
--
return (expression)
end rising_edge;
```

- Formal parameters and mode
- Functions cannot modify parameters
- Types of formals and actuals must match except for formals which are constants (default)
- Wait statements are not permitted in a function!

Placement of Functions

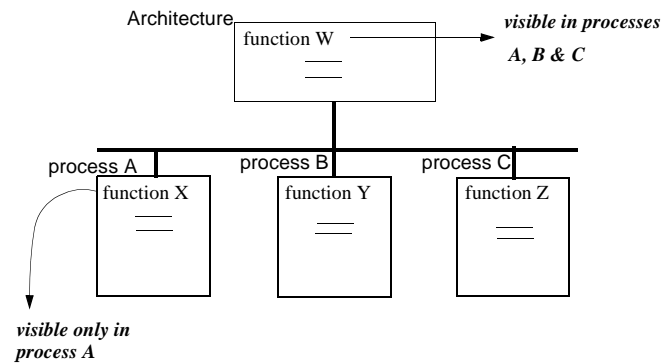

- When used by multiple design entities place functions in packages

2

Function: Example

```
architecture behavioral of dff is
  function rising_edge (signal clock : std_logic) return boolean is
    variable edge : boolean:= FALSE;
  begin
    edge := (clock = '1' and clock'event);
    return (edge);
  end rising_edge;

begin
  output: process
  begin
    wait until (rising_edge (Clk) );

    Q <= D after 5 ns;
    Qbar <= not D after 5 ns;

  end process output;
end behavioral;
```

Architecture
Declarative
Region

3

Function: Example


```
function to_bitvector (svalue : std_logic_vector) return bit_vector is
  variable outvalue : bit_vector (svalue'length-1 downto 0);
begin
  for i in svalue'range loop -- scan all elements of the array
    case svalue (i) is
      when '0' => outvalue (i) := '0';
      when '1' => outvalue (i) := '1';
      when others => outvalue (i) := '0';
    end case;
  end loop;
  return outvalue;
end to_bitvector
```

- Type conversion functions
 - interoperability
- Use of attributes for flexible function definitions
- Browse the vendor supplied packages for many examples

4

Implementation of Signals

 
- The structure of a signal assignment statement
 - *signal* <= (*value expression after time expression*)
 - RHS is referred to as a *waveform element*
- Every signal has associated with it a *driver*



- holds the current and future values of the signal - a *projected waveform*
- signal assignment statements modify the driver of a signal
- value of a signal is the value at the head of the driver
- note the hardware analogy

5


Shared Signals

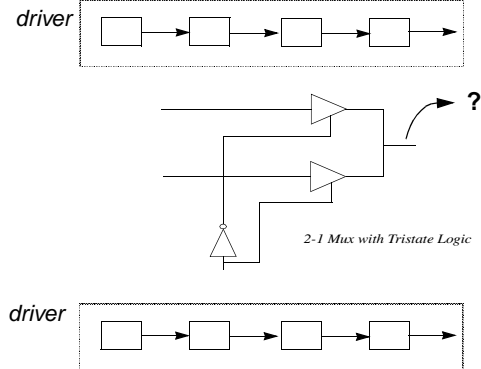

- How do we model the state of a wire?
- Rules for determining the signal value is captured in the resolution function

6

Resolved Signals

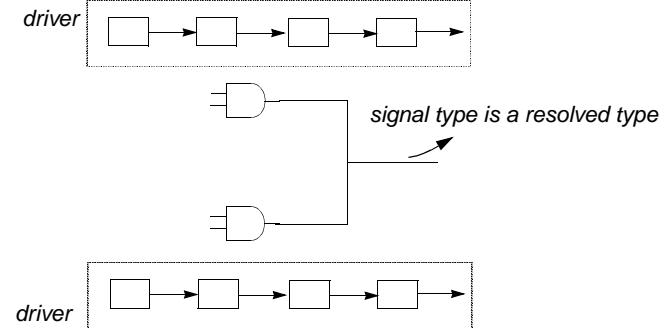

- Resolution function is invoked whenever an event occurs on this signal
- Resolution must be an associative operation

7

Resolved Types: std_logic

```
type std_ulogic is (
  'U', -- Uninitialized
  'X', -- Forcing Unknown
  '0', -- Forcing 0
  '1', -- Forcing 1
  'Z', -- High Impedance
  'W', -- Weak Unknown
  'L', -- Weak 0
  'H', -- Weak 1
  '-' -- Don't care
);
```

supports only single drivers

```
function resolved (s : std_ulogic_vector) return
std_ulogic;
```

```
subtype std_logic is resolved std_ulogic;
```

supports multiple drivers

8

Resolution Function: std_logic & resolved()


- resolving values for std_logic types

	U	X	0	1	Z	W	L	H	-
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	X	0	0	0	0	X
1	U	X	X	1	1	1	1	1	X
Z	U	X	0	1	Z	W	L	H	X
W	U	X	0	1	W	W	W	W	X
L	U	X	0	1	L	W	L	W	X
H	U	X	0	1	H	W	W	H	X
-	U	X	X	X	X	X	X	X	X

- Pairwise resolution of signal values from multiple drivers
- Resolution operation must be associative

9

Example

 

- Multiple components driving a shared error signal
- Signal value is the logical OR of the driver values

10

A Complete Example

```
library IEEE;
use IEEE.std_logic_1164.all;

entity mcm is
end mcm;

architecture behavioral of mcm is
function wire_or (sbus :std_ulogic_vector)
return std_ulogic;
begin
for i in sbus'range loop
if sbus (i) = '1' then
return '1';
end if;
end loop;
return '0';
end wire_or;

subtype wire_or_logic is wire_or
std_ulogic;
signal error_bus : wire_or_logic;
begin
Chip1: process
--..
error_bus <= '1' after 2 ns;
--..
end process Chip1;
Chip2: process
begin
--..
error_bus <= '0' after 2 ns;
--..
end process Chip2;
end behavioral;
```

- Use of unconstrained arrays and associative operations

11

Summary: Essentials of Functions

- Placement of functions
- Formal parameters
- Check the source listings of packages for examples of many different functions

12

Essentials of Procedures

```
procedure read_vld (variable f: in text; v :out std_logic_vector)
--declarative region: declare variables local to the procedure
--
begin
-- body
--
end read_vld;
```

- parameters may be of mode **in** (read only) and **out** (write only)
- default class of input parameters is constant
- default class of output parameters is variable
- variables declared within procedure are initialized on each call

13

Procedures: Placement

architecture behavioral of cpu is

```
--
-- decalarative region
-- procedures can be placed in their entirety here
```

→ *visible to all processes*

begin

```
process_a: process
-- declarative region of a process
-- procedures can be placed here
```

→ *visible only within process_a*

begin

```
--
-- process body
--
```

end process_a;

```
process_b: process
--declarative regions
```

begin


```
-- process body
--
```

end process_b;

end behavioral;

14

Placement of Procedures

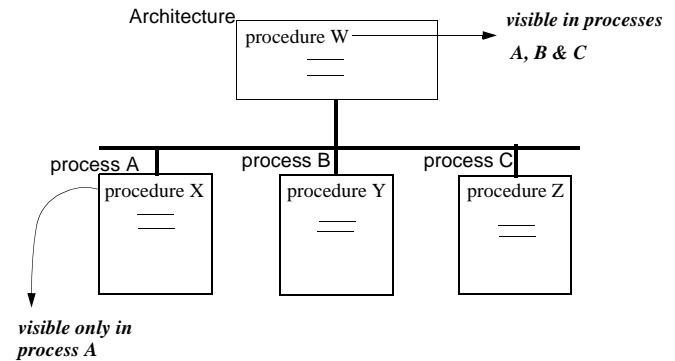

- placement of procedures determines visibility in its usage

15

Procedures and Signals

procedure mread (address : **in** std_logic_vector (2 **downto** 0));

signal R : **out** std_logic;

signal S : **in** std_logic;

signal ADDR : **out** std_logic_vector (2 **downto** 0);

signal data : **out** std_logic_vector (31 **downto** 0)) **is**

begin

ADDR <= address;

R <= '1';

wait until S = '1';

data <= DO;


R <= '0';

end mread;

- procedures can make assignments to signals passed as input parameters
- procedures may not have a wait statement if the encompassing process has a sensitivity list
- procedures may modify signals not in the parameter list, e.g., ports

16

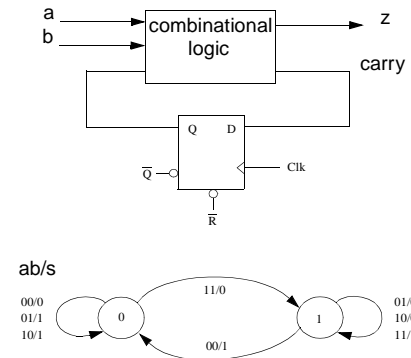Concurrent vs. Sequential Procedure Calls



- Example: bit serial adder

17

Concurrent Procedure Calls

```

architecture structural of serial_adder is
  component comb
    port (a, b, c_in : in std_logic;
          z, carry : out std_logic);
  end component;

  procedure dff (signal d, clk, reset : in std_logic;
                 signal q, qbar : out std_logic) is
  begin
    if (reset = '0') then
      q <= '0' after 5 ns;
      qbar <= '1' after 5 ns;
    elsif (clk'event and clk = '1') then
      q <= d after 5 ns;
      qbar <= (not D) after 5 ns;
    end if;
  end dff;

  signal s1, s2 : std_logic;

```

18

Equivalent Sequential Procedure Call

```

architecture structural of serial_adder is
  component comb
    port (a, b, c_in : in std_logic;
          z, carry : out std_logic);
  end component;


  procedure dff (signal d, clk, reset : in std_logic;
                 signal q, qbar : out std_logic) is
  begin
    if (reset = '0') then
      q <= '0' after 5 ns;
      qbar <= '1' after 5 ns;
    elsif (clk'event and clk = '1') then
      q <= d after 5 ns;
      qbar <= (not D) after 5 ns;
    end if;
  end dff;

  signal s1, s2 : std_logic;

```

19

Subprogram Overloading

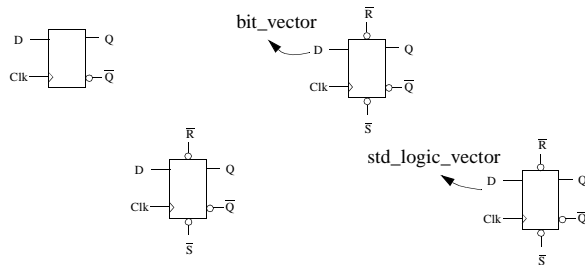

- hardware components differ in number of inputs and the type of input signals
- model each component by a distinct procedure
 - procedure naming becomes tedious

20

Subprogram Overloading

- consider the following procedures for the previous components
 - dff_bit (clk, d, q, qbar)
 - asynch_dff_bit (clk, d, q, qbar, reset, clear)
 - dff_std (clk, d, q, qbar)
 - asynch_dff_std (clk, d, q, qbar, reset, clear)
- all of the previous components can use the same name --> subprogram overloading
- the proper procedure can be determined based on the arguments of the call

21

Essentials of Packages

- Package Declaration
 - declaration of the functions, procedures, and types that are available in the package
 - serves as a package interface
 - only declared contents are visible for external use
- note the behavior of the **use** clause
- Package body
 - implementation of the functions and procedures declared in the package header

22

Example: Package Header std_logic_1164

```
package std_logic_1164 is
  type std_ulogic is ('U', -- Uninitialized
    'X', -- Forcing Unknown
    '0', -- Forcing 0
    '1', -- Forcing 1
    'Z', -- High Impedance
    'W', -- Weak Unknown
    'L', -- Weak 0
    'H', -- Weak 1
    '-' -- Don't care
  );
  type std_ulogic_vector is array (natural range <>) of std_ulogic;

  function resolved (s : std_ulogic_vector) return std_ulogic;
  subtype std_logic is resolved std_ulogic;

  type std_logic_vector is array (natural range <>) of std_logic;

  function "and" (l, r : std_logic_vector) return std_logic_vector;
  --..<rest of the package definition>
end std_logic_1164;
```

23


Example: Package Body

```
package body my_package is
  --
  -- type definitions, functions, and procedures
  --
end my_package;
```

- Packages are typically compiled into libraries
- New types must have associated definitions for operations such as logical operations (e.g., and, or) and arithmetic operations (e.g., +, *)
- Examine the package std_logic_1164 stored in library IEEE

24

Essentials of Libraries

 


- Design units are analyzed (compiled) and placed in libraries
- Logical library names map to physical directories
- Libraries STD and WORK are implicitly declared

25

Design Units

Primary Design Units

 

- Distinguish the primary design units

26

Visibility Rules

file.vhd

```
library IEEE;
use IEEE.std_logic_1164.all;
entity design-1 is
.....

library IEEE;
use IEEE.std_logic_1164.rising_edge;
entity design-2 is
.....
```

- when multiple design units are in the same file visibility of libraries and packages must be established for each **primary** design unit (entity, package header, configuration) separately!
- The **use** clause may selectively establish visibility, e.g., only the function `rising_edge()` is visible within entity design-2

27

Further reading

- VHDL Starter's Guide, Sudhakar Yalamanchili
- Check the [VHDL references](#) link from the course web page
- Look at the on-line documentation available with ISE – there is a huge VHDL manual
- Read/copy the online manual placed in the [VHDL manual](#) link of the course web page

Homework

1. Download and install WebPack and ModelSim as described on the [VHDL references](#) course web page,
OR
Access the ISE Project Manager from a *vmware* enabled school Linux workstation;
- AND
2. Familiarize yourself with the design environment by completing the Tutorial and testing the designs we have discussed in lectures.