

L06: ALU Design

Adapted from:

CS152: Computer Architecture and Engineering
Dave Patterson (www.cs.berkeley.edu/~patterson)

Copyright 1997 UCB

Overview

- Integer Multiplier
- Shifter
- Integer Divider
- Floating Point Representation & Operations (self study)

COMP3211/9211

2004 S2 L06 P2

MIPS arithmetic instructions

Instruction	Example	Meaning	Comments
add	add \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; exception possible
subtract	sub \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; exception possible
add immediate	addi \$1,\$2,100	$\$1 = \$2 + 100$	+ constant; exception possible
add unsigned	addu \$1,\$2,\$3	$\$1 = \$2 + \$3$	3 operands; no exceptions
subtract unsigned	subu \$1,\$2,\$3	$\$1 = \$2 - \$3$	3 operands; no exceptions
add imm. unsign.	addiu \$1,\$2,100	$\$1 = \$2 + 100$	+ constant; no exceptions
multiply	mult \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit signed product
multiply unsigned	multu \$2,\$3	Hi, Lo = $\$2 \times \3	64-bit unsigned product
divide	div \$2,\$3	Lo = $\$2 \div \3 , Hi = $\$2 \bmod \3	Lo = quotient, Hi = remainder
divide unsigned	divu \$2,\$3	Lo = $\$2 \div \3 , Hi = $\$2 \bmod \3	Unsigned quotient & remainder
Move from Hi	mfhi \$1	$\$1 = \text{Hi}$	Used to get copy of Hi
Move from Lo	mflo \$1	$\$1 = \text{Lo}$	Used to get copy of Lo

MULTIPLY (unsigned)

- Paper and pencil example (unsigned):

Multiplicand	1000
Multiplier	1001
	1000
	0000
	0000
	1000
Product	01001000

- m bits x n bits = m+n bit product
- Binary makes it easy:
 - 0 => place 0 (0 x multiplicand)
 - 1 => place a copy (1 x multiplicand)
- 4 versions of multiply hardware & algorithm:
 - successive refinement


COMP3211/9211

2004 S2 L06 P3

COMP3211/9211

2004 S2 L06 P4

 Unsigned Combinational Multiplier (ver 0)




- Stage i accumulates $A * 2^i$ if $B_i == 1$
- Q: How much hardware for 32 bit multiplier? Critical path?

COMP3211/9211

2004 S2 L06 P5

How does it work?

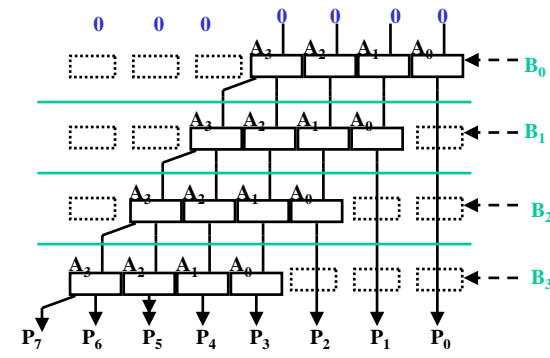


- at each stage shift A left (x 2)
- use next bit of B to determine whether to add in shifted multiplicand
- accumulate 2n bit partial product at each stage

COMP3211/9211

2004 S2 L06 P6

Unsigned shift-add multiplier (version 1)

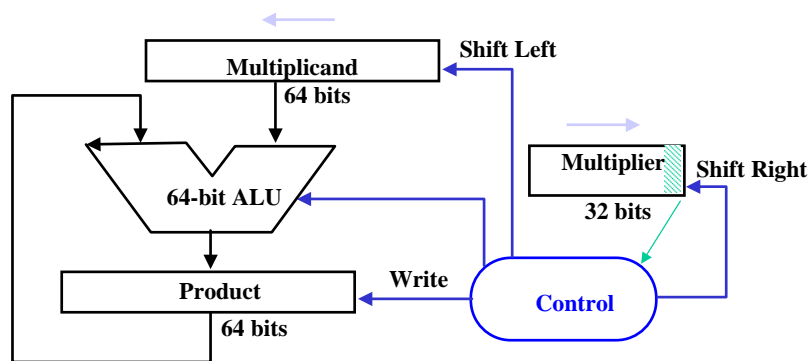- 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg




Multiplier = datapath + control

COMP3211/9211

2004 S2 L06 P7

Multiply Algorithm Version 1

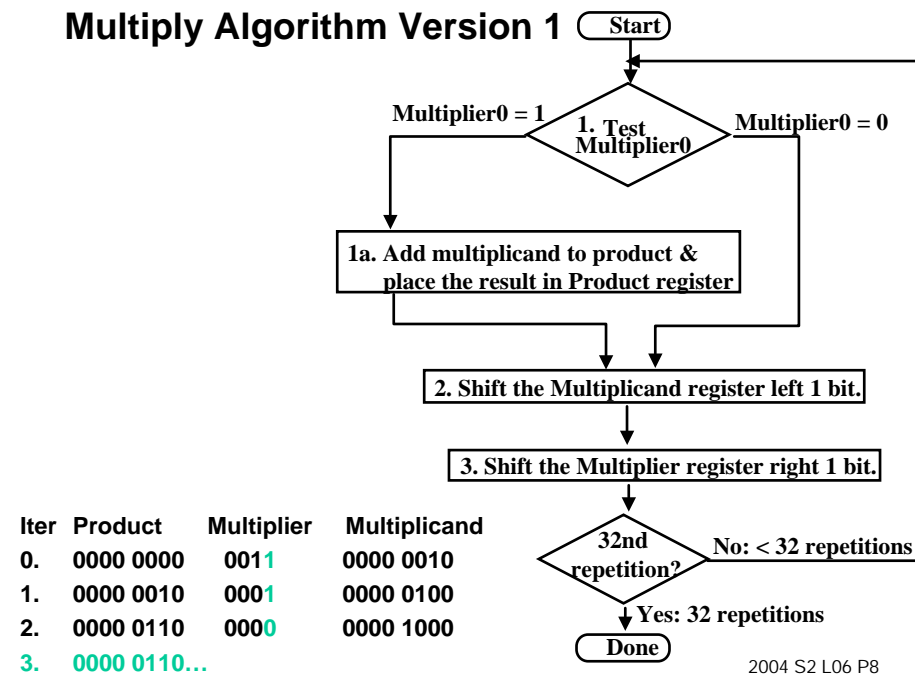


2004 S2 L06 P8

Observations on Multiply Version 1


- 1 clock per cycle => 2n clocks for n-bit multiply
 - Add is 5:1 to 100:1 times more popular than mult
 - But slow op will affect performance significantly
- 1/2 bits in multiplicand always 0
=> 64-bit adder is wasted
- 0's inserted in left of multiplicand as shifted
=> least significant bits of product never changed once formed
- Instead of shifting multiplicand to left, shift product to right?

MULTIPLY HARDWARE Version 2

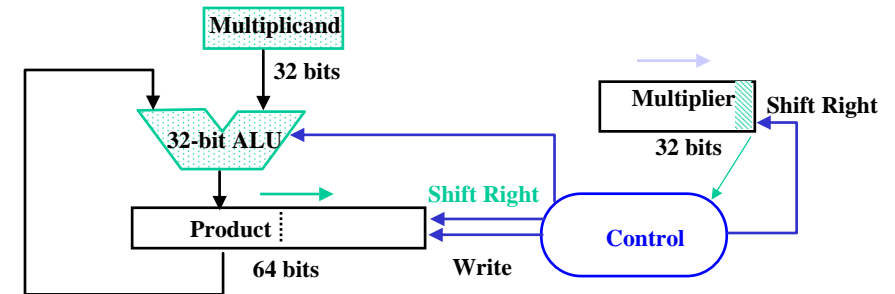
- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, 32-bit Multiplier reg



Multiply Algorithm Version 2

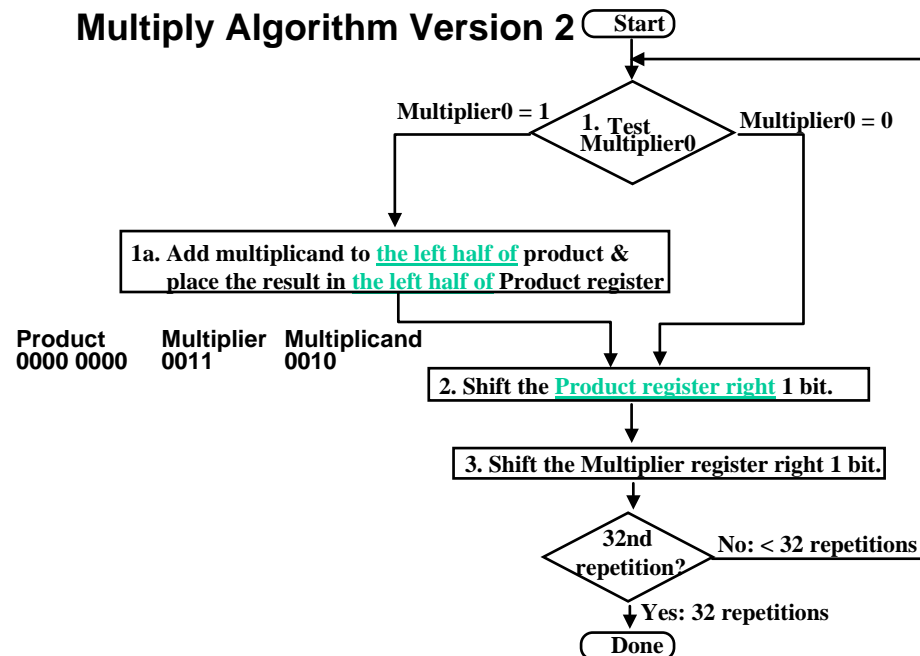

What's going on?

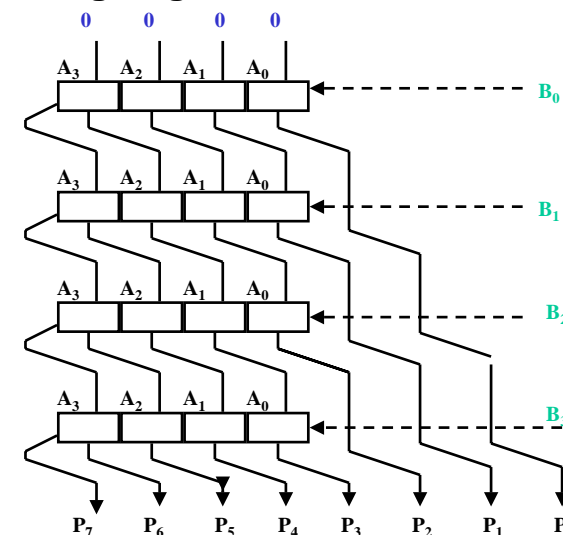


- Multiplicand stay's still and product moves right

Break

- 5-minute Break/ Do it yourself Multiply

Multiplier	Multiplicand	Product
0011	0010	0000 0000

Multiply Algorithm Version 2

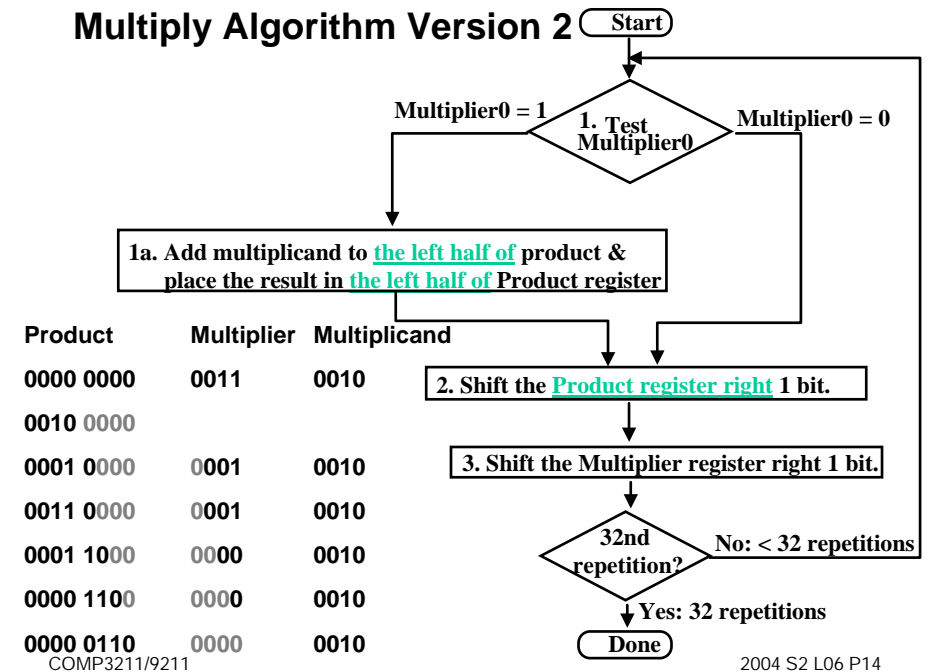



Observations on Multiply Version 2

- Product register wastes space that exactly matches size of multiplier
=> combine Multiplier register and Product register

MULTIPLY HARDWARE Version 3

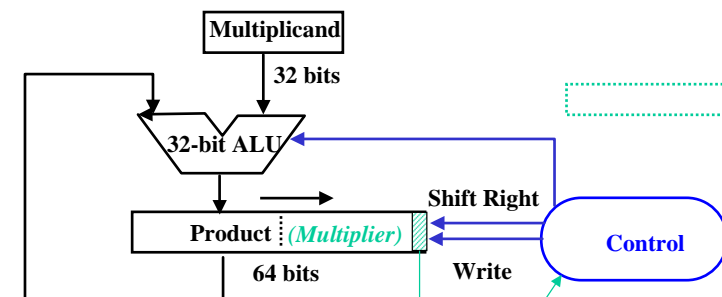- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



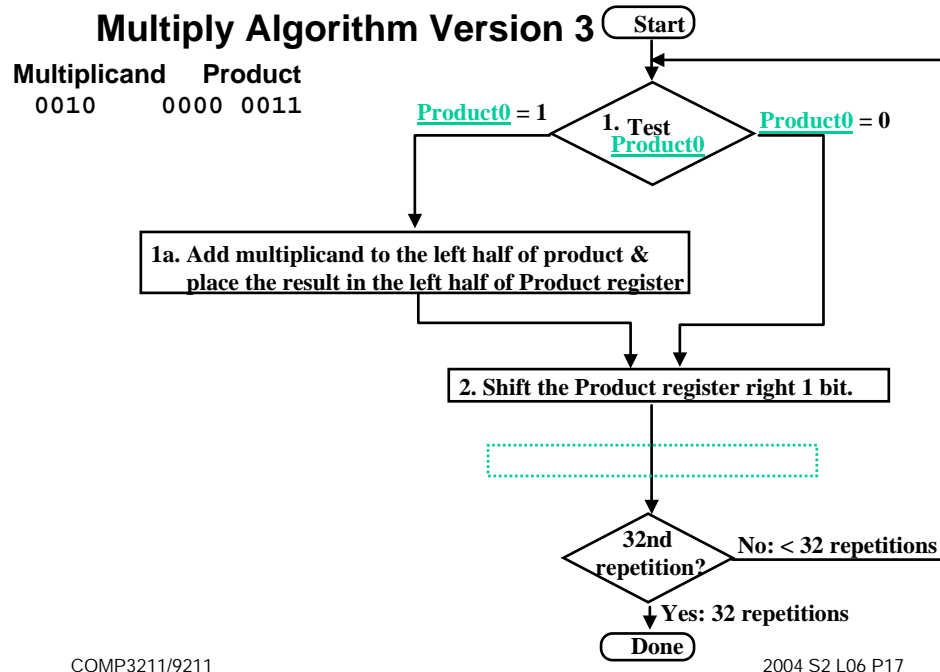

Observations on Multiply Version 3

- 2 steps per bit because Multiplier & Product combined
- MIPS registers Hi and Lo are left and right half of Product
- Gives us MIPS instruction MultU
- How can you make it faster?
- What about signed multiplication?
 - easiest solution is to make both positive & remember whether to complement product when done (leave out the sign bit, run for 31 steps)
 - apply definition of 2's complement
 - need to sign-extend partial products and subtract at the end
 - Booth's Algorithm is elegant way to multiply signed numbers using same hardware as before and save cycles
 - can handle multiple bits at a time

COMP3211/9211

2004 S2 L06 P18

Motivation for Booth's Algorithm

Example $2 \times 6 = 0010 \times 0110$:

	0010	
x	0110	
+	0000	shift (0 in multiplier)
+	0010	add (1 in multiplier)
+	0010	add (1 in multiplier)
+	0000	shift (0 in multiplier)
	00001100	

ALU with add or subtract gets same result in more than one way:

$$6 = -2 + 8$$

$$0110 = -00010 + 01000 = 11110 + 01000$$


For example

	0010	
x	0110	
	0000	shift (0 in multiplier)
-	0010	sub (first 1 in multpl.)
	0000	shift (mid string of 1s)
+	0010	add (prior step had last 1)
	00001100	

COMP3211/9211 2004 S2 L06 P19

Booth's Algorithm

 Replace a string of 1s in multiplier with an initial subtract when we first see a one and then later add for the bit after the last one



Current Bit	Bit to the Right	Explanation	Example	Op
1	0	Begins run of 1s	000111 <u>1</u> 000	sub
1	1	Middle of run of 1s	00011 <u>1</u> 1000	none
0	1	End of run of 1s	000 <u>1</u> 111000	add
0	0	Middle of run of 0s	00 <u>0</u> 1111000	none

Originally for Speed (when shift was faster than add)

$$\begin{array}{r}
 -1 \\
 + 10000 \\
 \hline
 01111
 \end{array}$$

COMP3211/9211

2004 S2 L06 P20

Booths Example (2 x 7)

Operation	Multiplicand	Product	Current bit Bit to right next?
0. initial value	0010	0000 0111 0	10 -> sub
1a. $P = P - m$	1110	+ 1110 1110 0111 0	shift P (sign ext)
1b.	0010	1111 0011 1	11 -> nop, shift
2.	0010	1111 1001 1	11 -> nop, shift
3.	0010	1111 1100 1	01 -> add
4a.	0010	+ 0010 0001 1100 1	shift
4b.	0010	0000 1110 0	done

COMP3211/9211

2004 S2 L06 P21

Booths Example (2 x -3)

Operation	Multiplicand	Product	Current bit Bit to right next?
0. initial value	0010	0000 1101 0	10 -> sub
1a. $P = P - m$	1110	+1110 1110 1101 0	shift P (sign ext)
1b.	0010	1111 0110 1	01 -> add
2a.		0001 0110 1	shift P
2b.	0010	0000 1011 0	10 -> sub
3a.	0010	1110 1011 0	shift
3b.	0010	1111 0101 1	11 -> nop
4a		1111 0101 1	shift
4b.	0010	1111 1010 1	done

COMP3211/9211

2004 S2 L06 P22

Some questions

How long does an n -bit multiply take with Booth's algorithm?

How long does it take to do m n -bit multiplications?

Can we do better?

MIPS logical instructions

Instruction	Example	Meaning	Comment
and	and \$1,\$2,\$3	$\$1 = \$2 \& \$3$	3 reg. operands; Logical AND
or	or \$1,\$2,\$3	$\$1 = \$2 \mid \$3$	3 reg. operands; Logical OR
xor	xor \$1,\$2,\$3	$\$1 = \$2 \oplus \$3$	3 reg. operands; Logical XOR
nor	nor \$1,\$2,\$3	$\$1 = \sim(\$2 \mid \$3)$	3 reg. operands; Logical NOR
and immediate	andi \$1,\$2,10	$\$1 = \$2 \& 10$	Logical AND reg, constant
or immediate	ori \$1,\$2,10	$\$1 = \$2 \mid 10$	Logical OR reg, constant
xor immediate	xori \$1,\$2,10	$\$1 = \sim\$2 \& \sim 10$	Logical XOR reg, constant
shift left logical	sll \$1,\$2,10	$\$1 = \$2 \ll 10$	Shift left by constant
shift right logical	srl \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right by constant
shift right arithm.	sra \$1,\$2,10	$\$1 = \$2 \gg 10$	Shift right (sign extend)
shift left logical	sllv \$1,\$2,\$3	$\$1 = \$2 \ll \$3$	Shift left by variable
shift right logical	srlv \$1,\$2,\$3	$\$1 = \$2 \gg \$3$	Shift right by variable
shift right arithm.	srav \$1,\$2,\$3	$\$1 = \$2 \gg \$3$	Shift right arith. by variable

COMP3211/9211

2004 S2 L06 P24


COMP3211/9211

2004 S2 L06 P23


Shifters

Two kinds:

logical-- value shifted in is always "0"

 

 
arithmetic-- on right shifts, sign extend




Note: these are single bit shifts. A given instruction might request 0 to 32 bits to be shifted!

Combinational Shifter from MUXes

Basic Building Block

 


8-bit right shifter

 

- What comes in the MSBs?
- How many levels for 32-bit shifter?
- What if we use 4-1 Muxes ?

 
General Shift Right Scheme using 16 bit example



If added Right-to-left connections could support Rotate (not in MIPS but found in ISAs)

Funnel Shifter


Instead Extract 32 bits of 64.

 

- Shift A by i bits (sa= shift right amount)
- Logical: Y = 0, X=A, sa=i
- Arithmetic? Y = _, X=_, sa=_
- Rotate? Y = _, X=_, sa=_
- Left shifts? Y = _, X=_, sa=_

Barrel Shifter

 Technology-dependent solutions: transistor per switch



COMP3211/9211

2004 S2 L06 P29

Divide: Paper & Pencil

```

      1001  Quotient
Divisor 1000 | 1001010  Dividend
      -1000
      ----
         10
         101
         1010
         -1000
          ----
             10  Remainder (or Modulo result)
    
```

See how big a number can be subtracted, creating quotient bit on each step

Binary $\Rightarrow 1 * \text{divisor}$ or $0 * \text{divisor}$

Dividend = Quotient x Divisor + Remainder

$\Rightarrow | \text{Dividend} | = | \text{Quotient} | + | \text{Divisor} |$


3 versions of divide, successive refinement

COMP3211/9211

2004 S2 L06 P30

DIVIDE HARDWARE Version 1

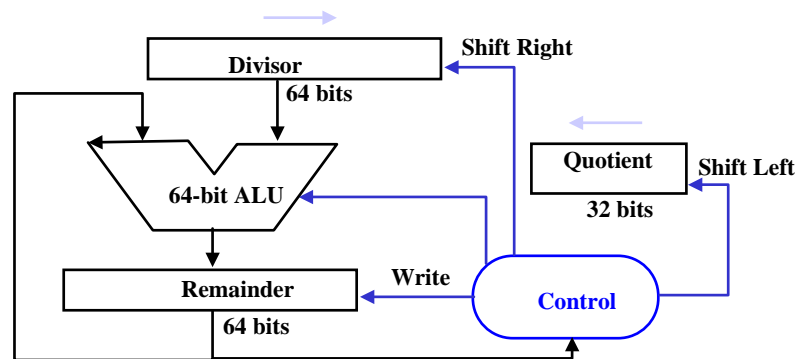- 64-bit Divisor reg, 64-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg




COMP3211/9211

2004 S2 L06 P31

Divide Algorithm Version 1

Takes $n+1$ steps for n -bit Quotient & Rem.

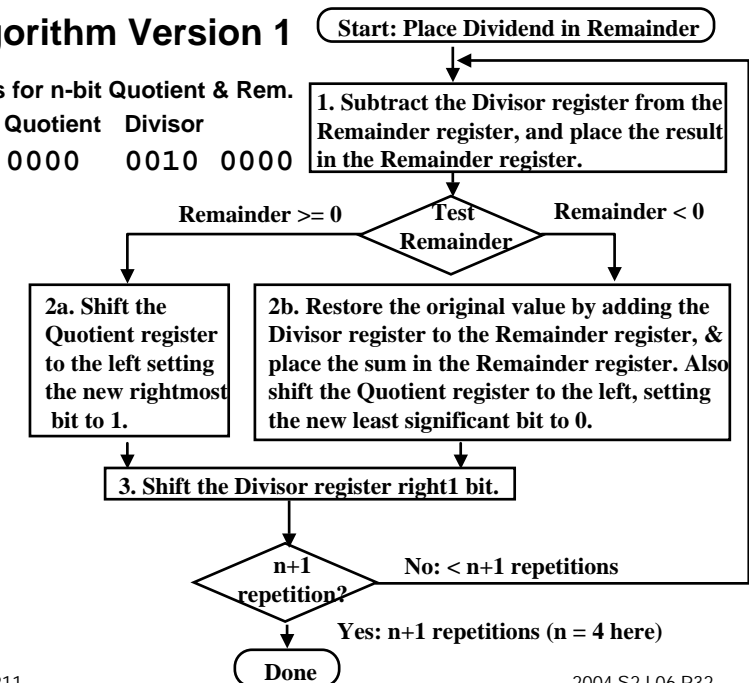Remainder Quotient Divisor
0000 0111 0000 0010 0000



COMP3211/9211


2004 S2 L06 P32

Observations on Divide Version 1

- 1/2 bits in divisor always 0
=> 1/2 of 64-bit adder is wasted
=> 1/2 of divisor is wasted
- Instead of shifting divisor to right, shift remainder to left?
- 1st step cannot produce a 1 in quotient bit (otherwise too big)
=> switch order to shift first and then subtract, can save 1 iteration


DIVIDE HARDWARE Version 2

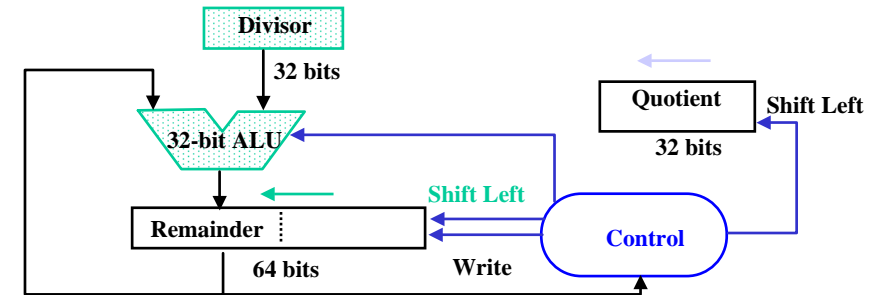- 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, 32-bit Quotient reg



Divide Algorithm Version 2

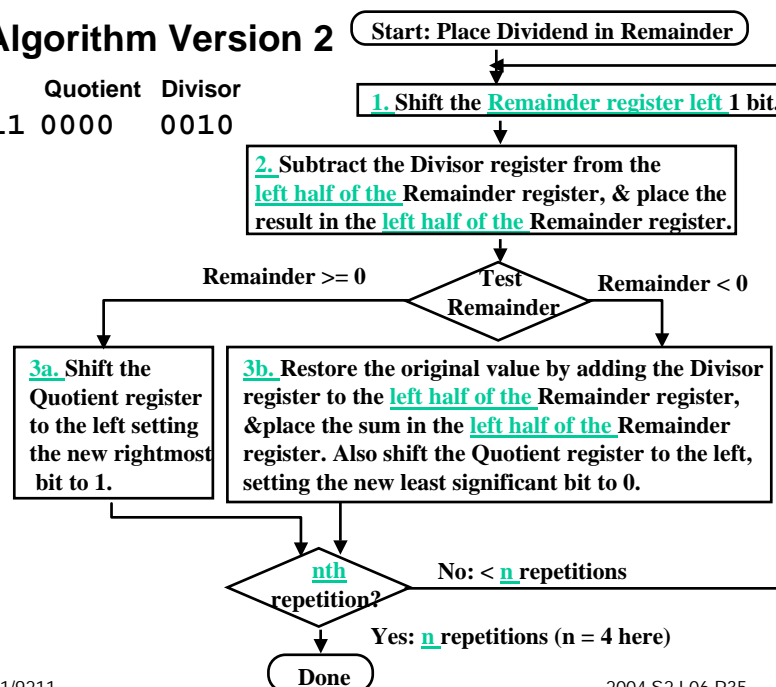Remainder Quotient Divisor
0000 0111 0000 0010




Observations on Divide Version 2

- Eliminate Quotient register by combining with Remainder as shifted left
 - Start by shifting the Remainder left as before.
 - Thereafter loop contains only two steps because the shifting of the Remainder register shifts both the remainder in the left half and the quotient in the right half
 - The consequence of combining the two registers together and the new order of the operations in the loop is that the remainder will be shifted left one time too many.
 - Thus a final correction step must shift back only the remainder in the left half of the register

DIVIDE HARDWARE Version 3

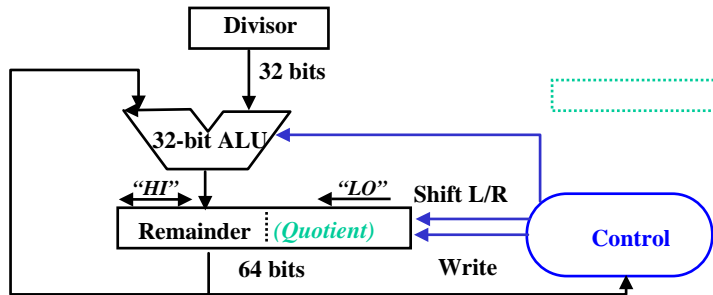- 32-bit Divisor reg, 32-bit ALU, 64-bit Remainder reg, (0-bit Quotient reg)




COMP3211/9211

2004 S2 L06 P37

Divide Algorithm Version 3

Remainder Divisor
0000 0111 0010

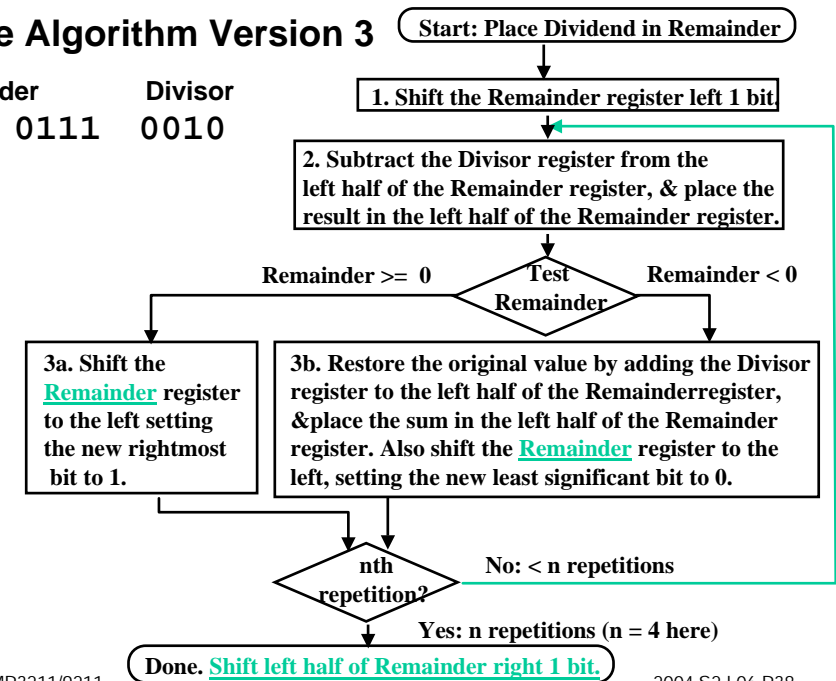

COMP3211/9211

2004 S2 L06 P38

Observations on Divide Version 3

- Same Hardware as Multiply: just need ALU to add or subtract, and 63-bit register to shift left or shift right
- Hi and Lo registers in MIPS combine to act as 64-bit register for multiply and divide
- Signed Divides: Simplest is to remember signs, make positive, and complement quotient and remainder if necessary
 - Note: Dividend and Remainder must have same sign
 - Note: Quotient negated if Divisor sign & Dividend sign disagree e.g., $-7 \div 2 = -3$, remainder = -1
- Possible for quotient to be too large: if divide 64-bit integer by 1, quotient is 64 bits ("called saturation")

COMP3211/9211

2004 S2 L06 P39

Summary

- Multiply: successive refinement to see final design
 - 32-bit Adder, 64-bit shift register, 32-bit Multiplicand Register
 - Booth's algorithm to handle signed multiplies
 - There are algorithms that calculate many bits of multiply per cycle (see exercises 4.36 to 4.39 in COD)
- Shifter: success refinement 1/bit at a time shift register to barrel shifter
- Divide can use same hardware as multiply: Hi & Lo registers in MIPS
- Floating point basically follows paper and pencil method of scientific notation using integer algorithms for multiply and divide of significands

COMP3211/9211

2004 S2 L06 P40