

L07: Single Cycle Datapath Design

Adapted from:


CS152: Computer Architecture and Engineering
Dave Patterson (www.cs.berkeley.edu/~patterson)

Copyright 1997 UCB

The Big Picture: The Performance Perspective

- Performance of a machine is determined by:

 - Instruction count
- Clock cycle time
- Clock cycles per instruction



- Processor design (datapath and control) will determine:

- Clock cycle time
- Clock cycles per instruction

- Today:

- Single cycle processor:
 - Advantage: One clock cycle per instruction
 - Disadvantage: long cycle time

COMP3211/9211

2004 S2 L07 P2

How to Design a Processor: step-by-step


1. Analyze instruction set \Rightarrow datapath requirements
 - the meaning of each instruction is given by the register transfers
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that affect the register transfer.
5. Assemble the control logic

COMP3211/9211

2004 S2 L07 P3

The MIPS Instruction Formats

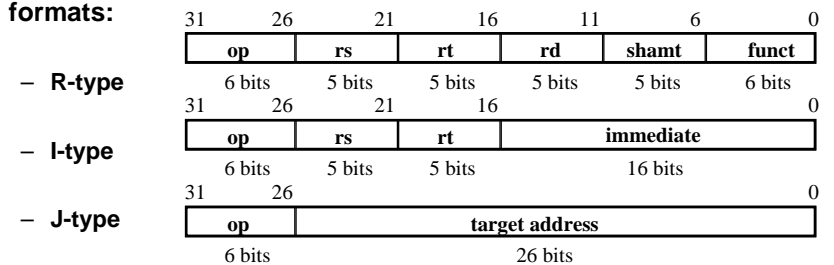- All MIPS instructions are 32 bits long. The three instruction formats:




- The different fields are:
 - op: operation of the instruction
 - rs, rt, rd: the source and destination register specifiers
 - shamt: shift amount
 - funct: selects the variant of the operation in the “op” field
 - address / immediate: address offset or immediate value
 - target address: target address of the jump instruction

COMP3211/9211


2004 S2 L07 P4

Step 1a: The MIPS-lite Subset for today

 
- **ADD and SUB**
 - `addU rd, rs, rt`
 - `subU rd, rs, rt`



 
- **OR Immediate:**
 - `ori rt, rs, imm16`



 - **LOAD and STORE Word**
 - lw rt, rs, imm16
 - sw rt, rs, imm16



- **BRANCH:**
 - beq rs, rt, imm16

 

Logical Register Transfers

- RTL gives the meaning of the instructions
- All start by fetching the instruction

MEM[PC] = op | rs | rt | rd | shamt | funct or
op | rs | rt | Imm16

inst **Register Transfers**

ADDU	$R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4;$
SUBU	$R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4;$
ORI	$R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16}); PC \leftarrow PC + 4;$
LOAD	$R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})]; PC \leftarrow PC + 4;$
STORE	$\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rt]; PC \leftarrow PC + 4;$
BEQ	if ($R[rs] == R[rt]$) then $PC \leftarrow PC + 4 + \text{sign_ext}(\text{Imm16})$ 00 else $PC \leftarrow PC + 4;$

Step 1: Requirements of the Instruction Set


- **Memory**
 - instruction & data
- **Registers (let's say 32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**

Step 2: Components of the Datapath


- **Combinational Elements**
- **Storage Elements**
 - Clocking methodology

Combinational Logic Elements (Basic Building Blocks)


- **Adder**

 

- **MUX**

 

- **ALU**

 


COMP3211/9211

2004 S2 L07 P9

Storage Element: Register (Basic Building Block)

- **Register**

 - Similar to the D Flip Flop except
 - N-bit input and output
 - Write Enable input
- Write Enable:
 - negated (0): Data Out will not change
 - asserted (1): Data Out will become Data In




COMP3211/9211

2004 S2 L07 P10

Storage Element: Register File

- **Register File consists of 32 registers:**

 - Two 32-bit output busses:
 - busA and busB
- One 32-bit input bus: busW



- **Register is selected by:**

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- **Clock input (CLK)**

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after “access time.”


COMP3211/9211

2004 S2 L07 P11

Storage Element: Memory

- **Memory (idealized)**

 - One input bus: Data In
- One output bus: Data Out



- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus


- **Clock input (CLK)**

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid \Rightarrow Data Out valid after “access time.”

COMP3211/9211

2004 S2 L07 P12

Clocking Methodology

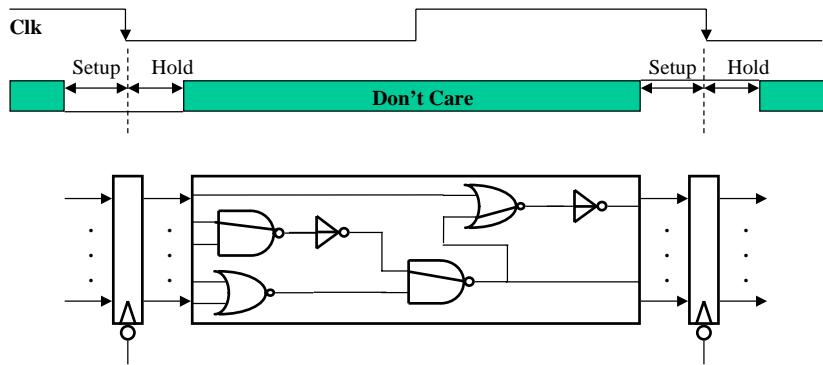

All storage elements are clocked by the same clock edge

Cycle Time \geq CLK-to-Q + Longest Delay Path + Setup + Clock Skew

– Clock skew = difference in arrival time of clock edges

$(\text{CLK-to-Q} + \text{Shortest Delay Path} - \text{Clock Skew}) > \text{Hold Time}$

Step 3

Register Transfer Requirements


→ Datapath Assembly

1. Instruction Fetch
2. Read Operands and Execute Operation

3a: Overview of the Instruction Fetch Unit

Common RTL operations:

 - a) At start of cycle, fetch the instruction: $\text{mem}[\text{PC}]$
- b) At end of cycle, update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$




3b: Add & Subtract


$R[\text{rd}] \leftarrow R[\text{rs}] \text{ op } R[\text{rt}]$

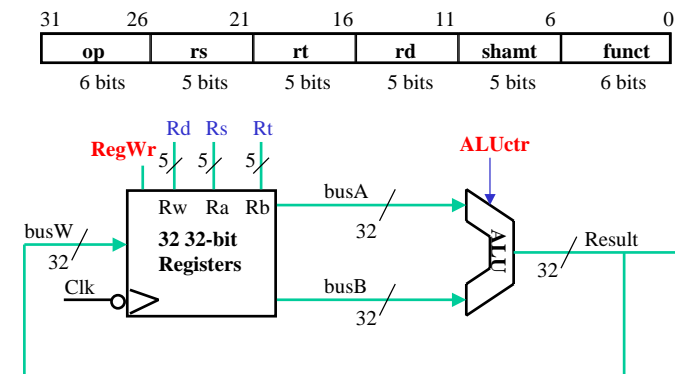Example: **addU rd, rs, rt**

- Ra, Rb, and Rw come from instruction's rs, rt, and rd fields
- ALUctr and RegWr: control logic after decoding the instruction



Register-Register Timing

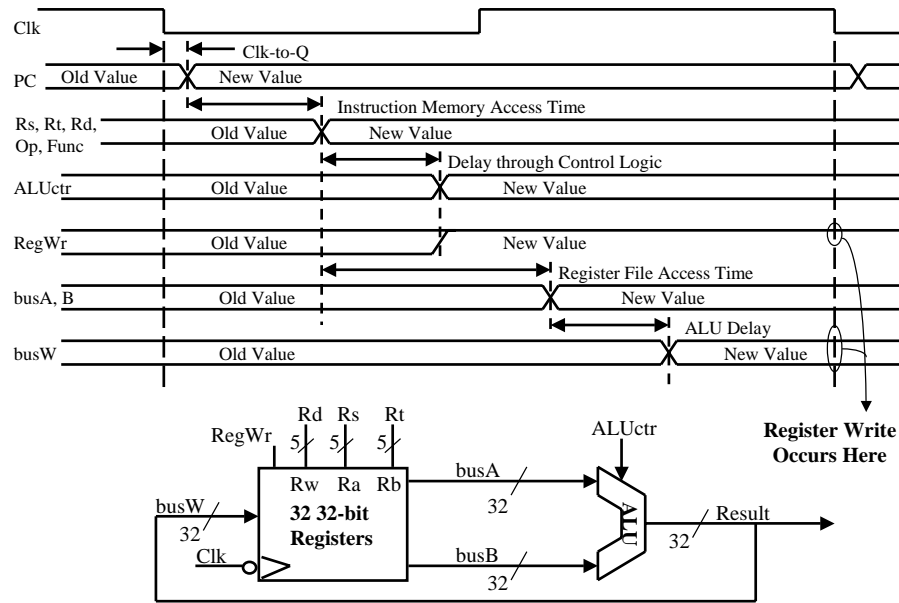


COMP3211/9211

2004 S2 L07 P17

3c: Logical Operations with Immediate
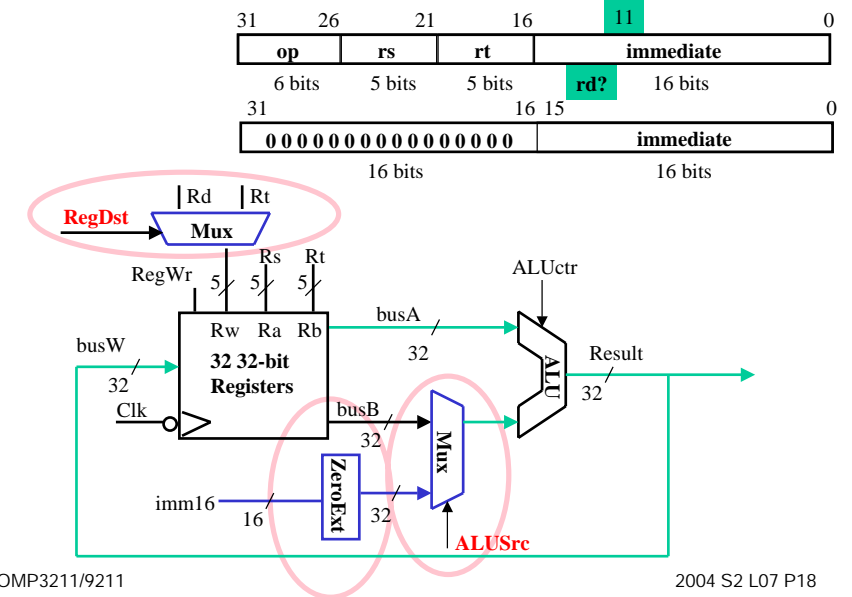
$$R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$$




COMP3211/9211

2004 S2 L07 P18

3d: Load Operations
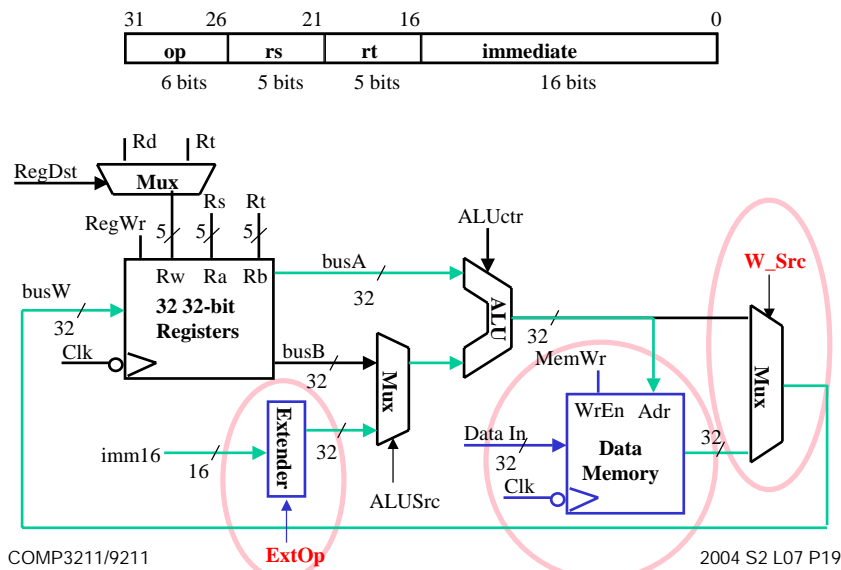
$$R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[imm16]] \quad \text{Example: lw rt, rs, imm16}$$




COMP3211/9211

2004 S2 L07 P19

3e: Store Operations

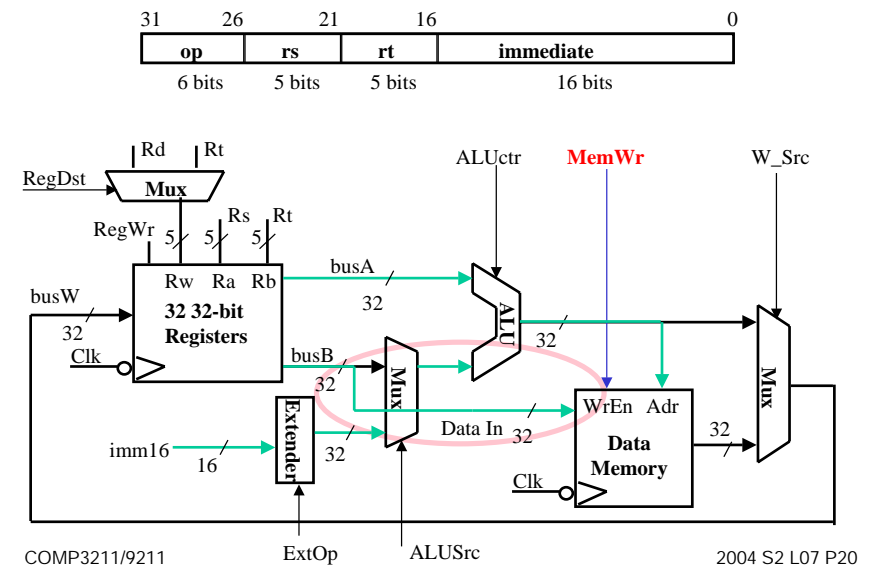
$$\text{Mem}[R[rs] + \text{SignExt}[imm16]] \leftarrow R[rt] \quad \text{Example: sw rt, rs, imm16}$$



COMP3211/9211

2004 S2 L07 P20

3f: The Branch Instruction

 

beq rs, rt, imm16

- mem[PC] **Fetch the instruction from memory**
- $\text{Equal} \leftarrow R[\text{rs}] == R[\text{rt}]$ **Calculate the branch condition**
- if (COND eq 0) **Calculate the next instruction's address**
 $\text{PC} \leftarrow \text{PC} + 4 + (\text{SignExt}(\text{imm16}) \times 4)$
 else
 $\text{PC} \leftarrow \text{PC} + 4$


COMP3211/9211

2004 S2 L07 P21

Datpath for Branch Operations

beq rs, rt, imm16


Datpath generates condition (equal)

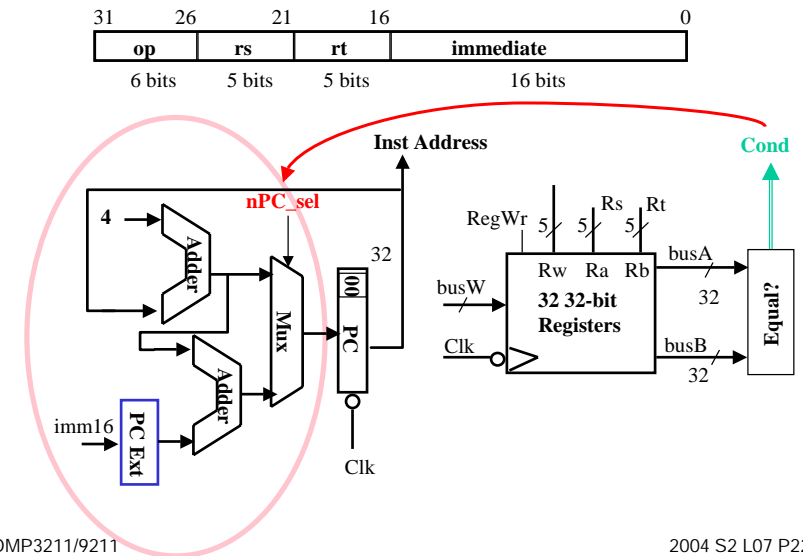

COMP3211/9211

2004 S2 L07 P22

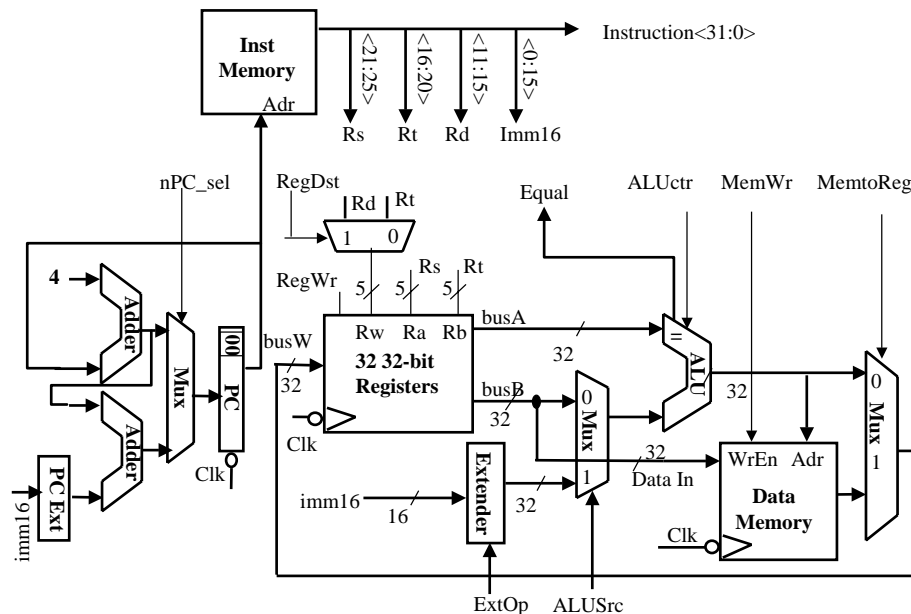Putting it All Together: A Single Cycle Datapath




COMP3211/9211

2004 S2 L07 P23

An Abstract View of the Critical Path

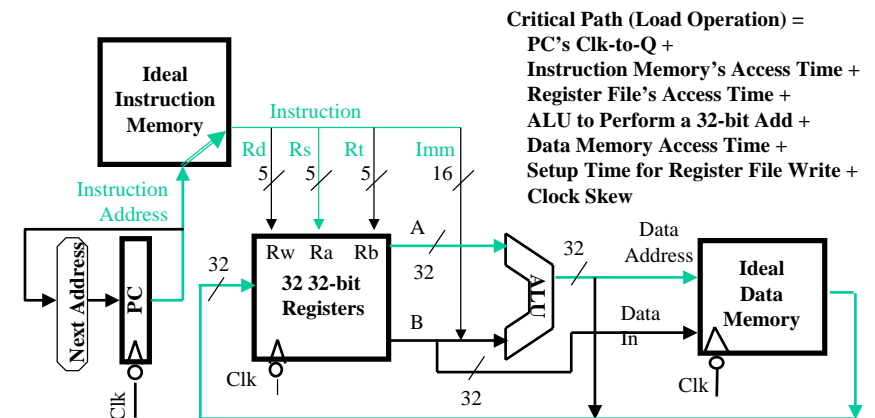- Register file and ideal memory:
 - The CLK input is a factor ONLY during write operation
 - During read operation, behave as combinational logic:
 - Address valid => Output valid after “access time.”




COMP3211/9211

2004 S2 L07 P24

Critical Path (Load Operation) =
 PC's Clk-to-Q +
 Instruction Memory's Access Time +
 Register File's Access Time +
 ALU to Perform a 32-bit Add +
 Data Memory Access Time +
 Setup Time for Register File Write +
 Clock Skew

Step 4: Given Datapath: RTL → Control

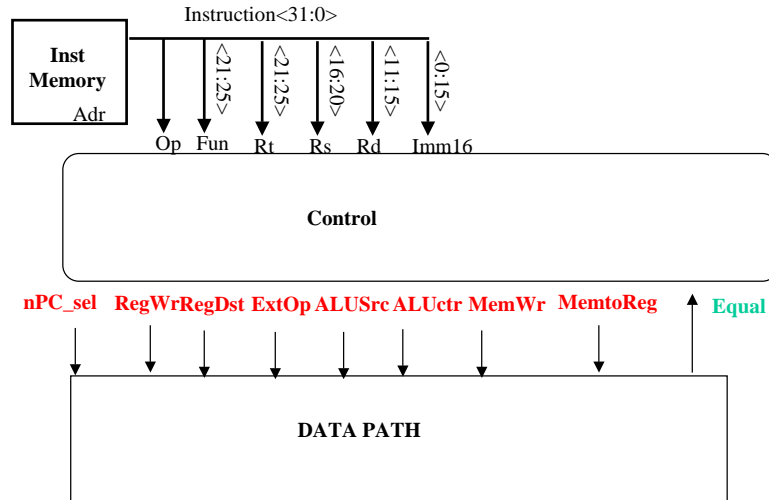


COMP3211/9211

2004 S2 L07 P25

Meaning of the Control Signals (see 3 slides back)

Rs, Rt, Rd and lmed16 hardwired into datapath

nPC_sel: 0 \Rightarrow PC \leftarrow PC + 4; 1 \Rightarrow PC \leftarrow PC + 4 + SignExt(Imm16) || 00

 


COMP3211/9211

2004 S2 L07 P26

Meaning of the Control Signals (see 4 slides back)

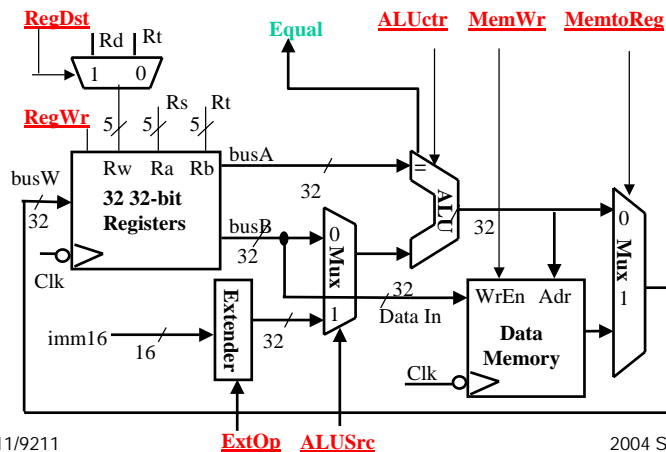- ExtOp: "zero", "sign"
- ALUSrc: 0 \Rightarrow regB; 1 \Rightarrow immed
- ALUctr: "add", "sub", "or"
- MemWr: write memory
- MemtoReg: 1 \Rightarrow Mem
- RegDst: 0 \Rightarrow "rt"; 1 \Rightarrow "rd"
- RegWr: write dest register



COMP3211/9211

2004 S2 L07 P27

Control Signals

inst Register Transfer

ADD R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4

ALUSrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"

SUB R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4

ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __

ORI R[rt] \leftarrow R[rs] + zero_ext(Imm16); PC \leftarrow PC + 4

ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __

LOAD R[rt] \leftarrow MEM[R[rs] + sign_ext(Imm16)]; PC \leftarrow PC + 4

ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __

STORE MEM[R[rs] + sign_ext(Imm16)] \leftarrow R[rs]; PC \leftarrow PC + 4

ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __

BEQ if (R[rs] == R[rt]) then PC \leftarrow PC + sign_ext(Imm16) || 00 else PC \leftarrow PC + 4

ALUSrc = __, Extop = __, ALUctr = __, RegDst = __, RegWr(?), MemtoReg(?), MemWr(?), nPC_sel = __

COMP3211/9211

2004 S2 L07 P28

Control Signals

inst **Register Transfer**

ADD $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

ALUsrc = RegB, ALUctr = "add", RegDst = rd, RegWr, nPC_sel = "+4"

SUB **R[rd] ← R[rs] – R[rt];** **PC ← PC + 4**

ALUsrc = RegB, ALUctr = “sub”, RegDst = rd, RegWr, nPC_sel = “+4”

ORI **R[rt] ← R[rs] + zero_ext(Imm16);** **PC ← PC + 4**

ALUsrc = Im, Extop = "Z", ALUctr = "or", RegDst = rt, RegWr, nPC_sel = "+4"

LOAD $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = "Sn", ALUctr = "add",
MemtoReg, RegDst = rt, RegWr, nPC_sel = "+4"**

STORE $\text{MEM}[\text{R}[\text{rs}] + \text{sign_ext}(\text{Imm16})] \leftarrow \text{R}[\text{rs}]; \quad \text{PC} \leftarrow \text{PC} + 4$

ALUsrc = Im, Extop = "Sn", ALUctr = "add", MemWr, nPC_sel = "+4"

BEO if (R[rs] == R[rt]) then PC \leftarrow PC + sign ext(Imm16) || 00 else PC \leftarrow PC + 4

nPC sel = EQUAL, ALUctr = “sub”

COMP3211/9211

2004 S2 L07 P29

Step 5: Logic for each control signal

```
nPC_sel ← if (OP == BEQ) then EQUAL
        else 0
```

ALUsrc \Leftarrow if (OP == "000000") then "regB"
else "immed"

```

ALUctr    ⇐ if (OP == "000000") then funct
              elseif (OP == ORi) then "OR"
              elseif (OP == BEQ) then "sub"
              else "add"

```

ExtOp ←

MemWr

MementoReq ←

RegWr _____

RegDst ← _____

COMP3211/9211

2004 S2 L07 P30

Step 5: Logic for each control signal

nPC_sel \Leftarrow if (OP == BEQ) then EQUAL else 0

ALUsrc \Leftarrow if (OP == "000000") then "regB"
else "immed"

```

ALUctr    ⇐ if (OP == "000000") then funct
              elseif (OP == ORi) then "OR"
              elseif (OP == BEQ) then "sub"
              else "add"

```

ExtOp \Leftarrow if (OP == ORi) then “zero” else “sign”

MemWr \Leftarrow (OP == Store)

MemtoReg \leftarrow (OP == Load)

RegWr \leftarrow if ((OP == Store) || (OP == BEQ)) then 0
 else 1

```


RegDst    ← if ((OP == Load) || (OP == ORi)) then 0
              else 1

```

COMP3211/9211

2004 S2 L07 P31

Example: Load Instruction

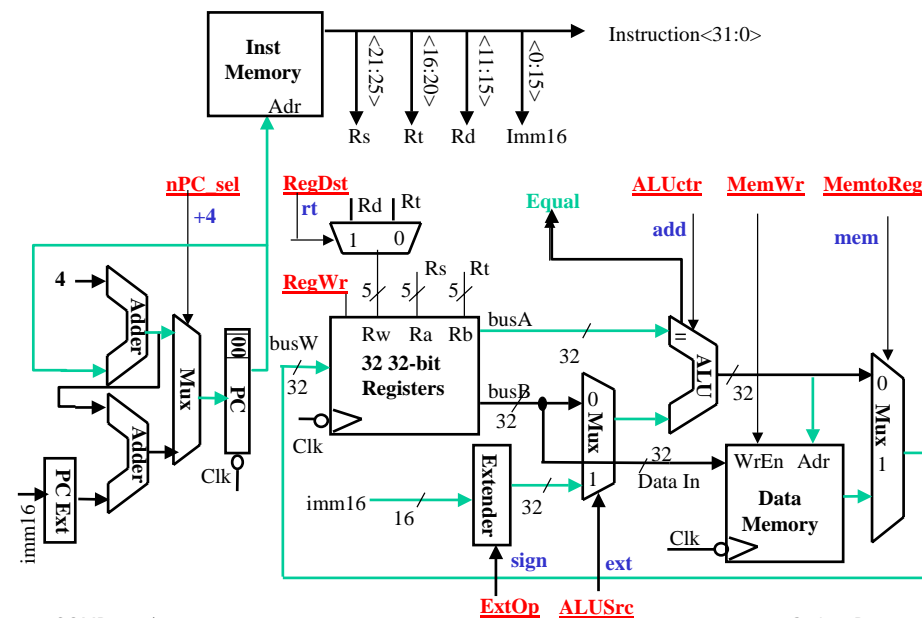

COMP3211/9211

2004 S2 L07 P32

Summary

- **5 steps to design a processor:**
 1. Analyze instruction set => datapath requirements
 2. Select set of datapath components & establish clock methodology
 3. Assemble datapath meeting the requirements
 4. Analyze implementation of each instruction to determine setting of control points that affect the register transfer.
 5. Assemble the control logic
- **MIPS makes it easier**
 - Instructions same size
 - Source registers always in same place
 - Immediates same size, location
 - Operations always on registers/immediates
- **Single cycle datapath => CPI=1, CCT => long**