

## ELEC2041

### Microprocessors and Interfacing

#### Lectures 31: Memory and Bus Organisation - I

<http://webct.edtec.unsw.edu.au/>

May 2005

Saeid Nooshabadi

saeid@unsw.edu.au

ELEC2041 lec31-mem-bus-1.1

Saeid Nooshabadi

## Overview


### Memory Interfacing

- Memory Type
- Memory Decoding
- D-RAM Access
- Making DRAM Access fast

ELEC2041 lec31-mem-bus-1.2

Saeid Nooshabadi

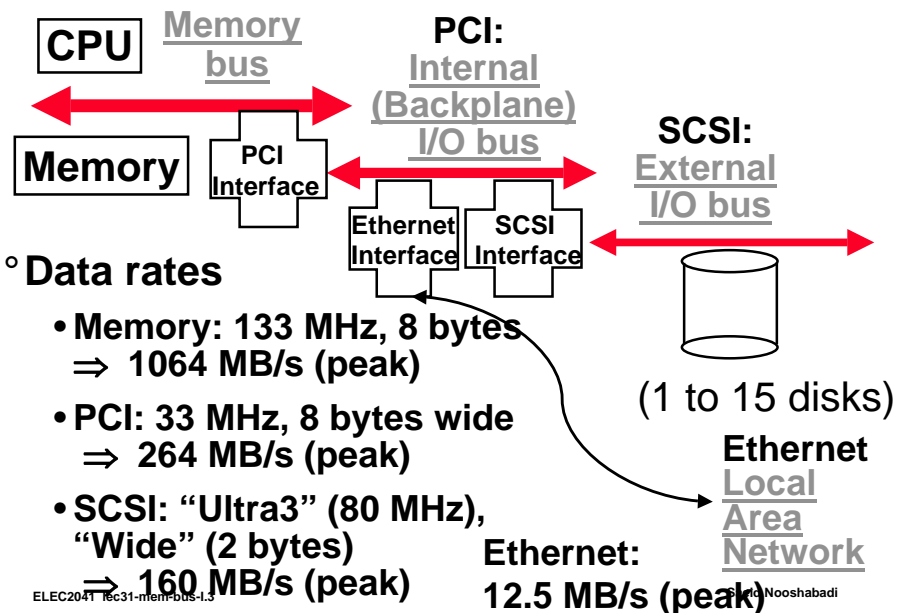
### Review: Buses in a PC: Connect a few devices



ELEC2041 lec31-mem-bus-1.3

Saeid Nooshabadi

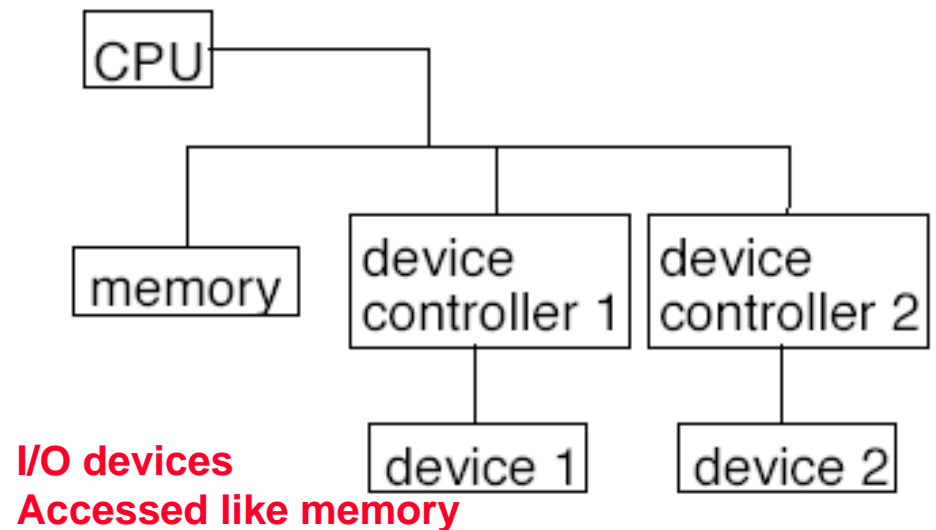
### Review: Computers with Memory Mapped I/O



ELEC2041 lec31-mem-bus-1.4

Saeid Nooshabadi

## Big Picture: A System on a Chip

 


**Integration of Core Processor and many sub-system micro-cells**

- **ARM7TDMI core**
  - **Cache RAM**
  - **Embedded Co-Processors**
  - **External Mem Interface**
  - **Low bandwidth I/O devices**
  - **Timers**
  - **I/O ports**
- Saeid Nooshabadi

**Saeid Nooshabadi**

# ARM System Architecture

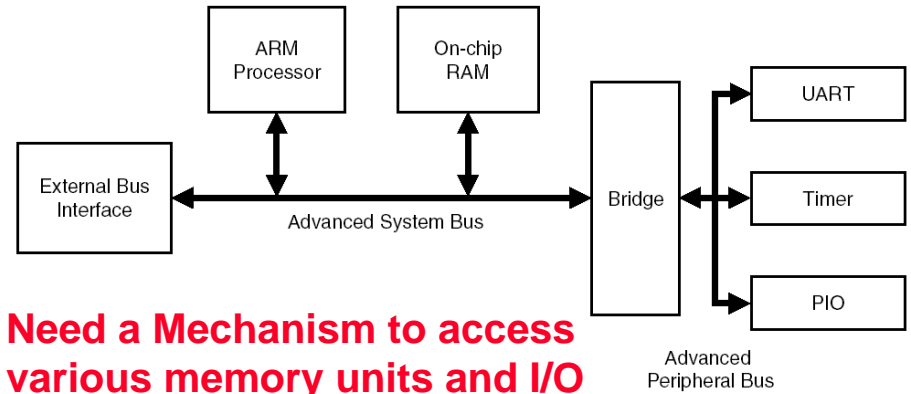


**Need a Mechanism to access various memory units and I/O devices, uniquely, to avoid access conflicts**

ELEC2041 lec31-mem-bus-l.6

**Saeid Nooshabadi**
 
## ARM System Architecture with Multiple Masters




**Need a Mechanism to allow various Processing units to access the Memory Bus without causing conflict**

ELEC2041 lec31-mem-bus-l.7

**Saeid Nooshabadi**


## ARM Core Interface Signals

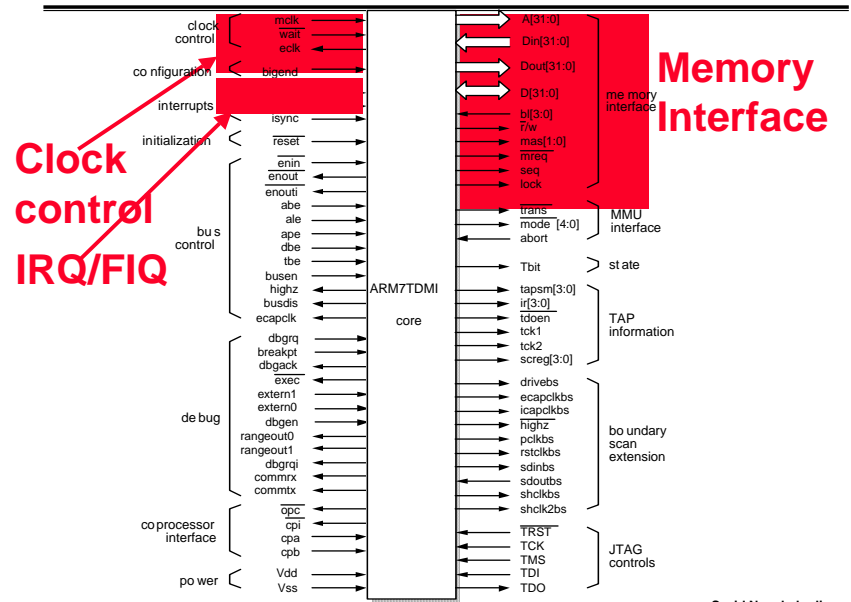

ELEC2041 lec31-mem-bus-l.8


**Saeid Nooshabadi**

## ARM Core Memory Interface Signals

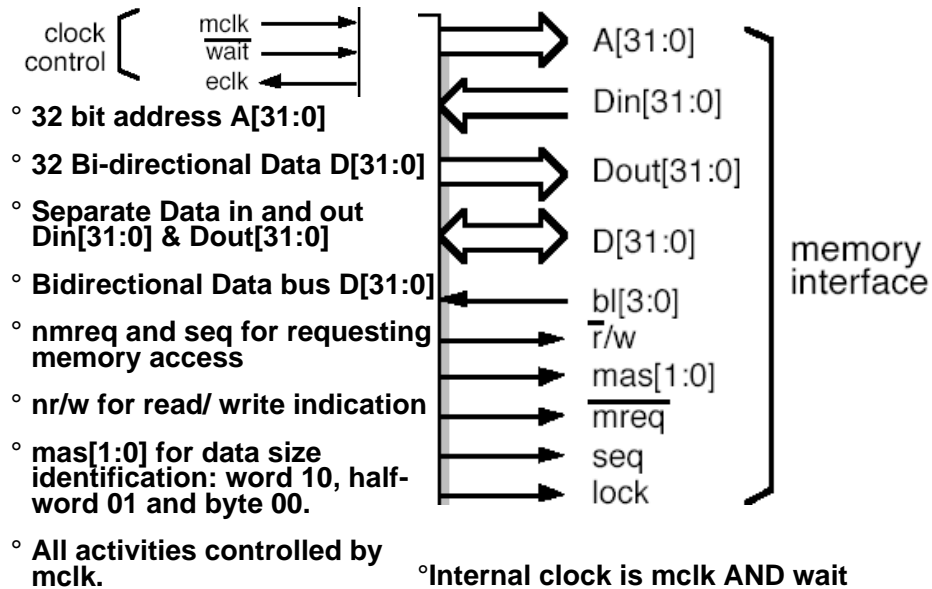


ELEC2041 lec31-mem-bus-1.9

## Simple Memory Interface

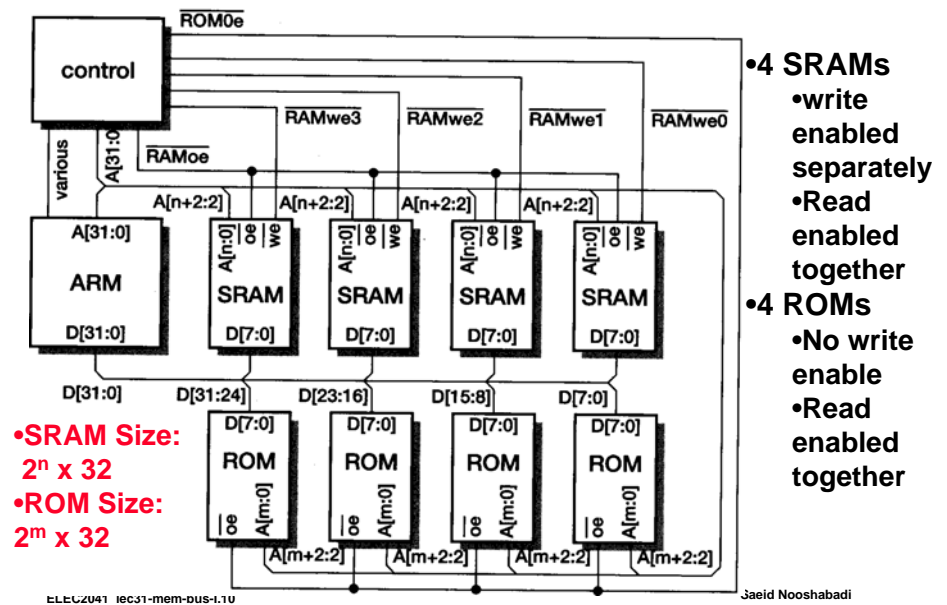

ELEC2041 lec31-mem-bus-1.10


## Simple Memory Decoder Control

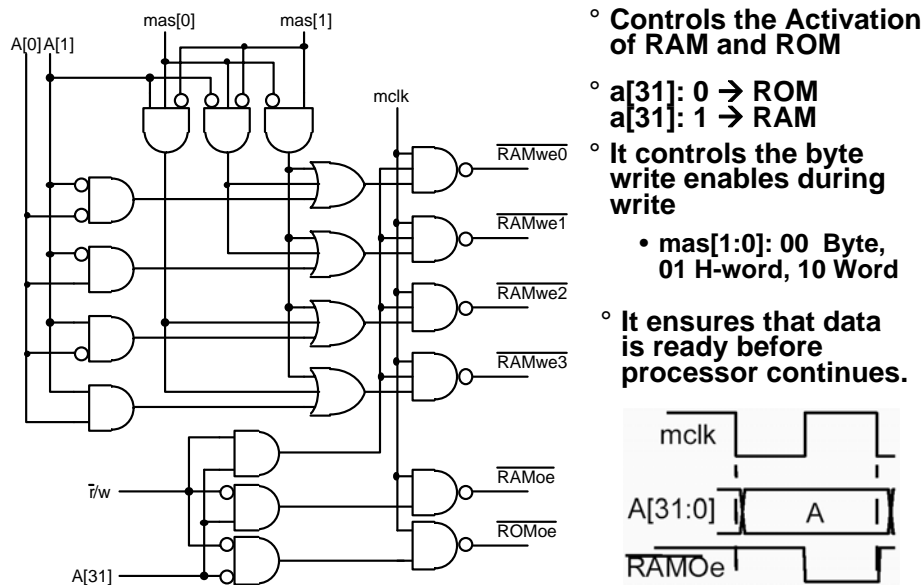

ELEC2041 lec31-mem-bus-1.12
 
## SRAM/ROM Memory Timing


- Address should be stable during the falling edge
- SRAM is fast, ROM is slow
- ROM needs more time. Slows the system
- Solutions?
  - Slow down the MCLK clock; loose performance
  - Use Wait states; more complex control



Saeid Nooshabadi
 
## ROM Wait Control State Transition


- ° ROM access requires 4 clock cycles
- ° RAM access is fast



ELEC2041 lec31-mem-bus-1.13

Saeid Nooshabadi
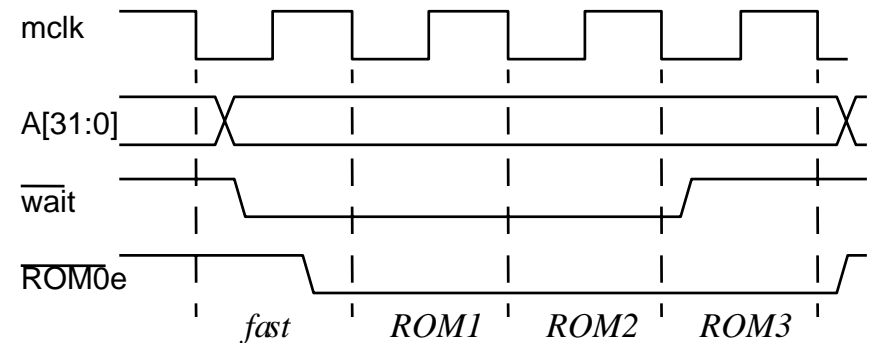
## Timing Diagram for for ROM Wait States




ELEC2041 lec31-mem-bus-1.14

Saeid Nooshabadi
 
## Improving Performance

- ° Processor internal operations cycles do not need access to memory
    - Mem. Access is much slower than internal operations.
    - Use wait states for mem Accesses
  - ° mreq = 1 internal operation
  - ° mreq = 0 memory access
- Internal Operations can run at max speed**



ELEC2041 lec31-mem-bus-1.15

Saeid Nooshabadi

## DRAM Interface


- ° Dynamic RAM Features:
  - much cheaper than SRAM
  - more capacity than SRAM
  - slower than SRAM
- ° Widely used in Computer Systems

ELEC2041 lec31-mem-bus-1.16

Saeid Nooshabadi
 
## DRAM Organisation

- Two dimensional matrix
- Bits are accesses by:
  - Accepting row and column addresses down the same multiplexed address bus
  - First Row address is presented and latched by ras signal
  - Next column address is presented and latched by cas signal



ELEC2041 lec31-mem-bus-1.17

Saeid Nooshabadi

## Making DRAM Access Fast


- Accessing data in the same row using cas-only access is 2 – 3 times faster
  - cas-only access does not activate the cell matrix
  - If next accesses is within the same row, a new column address may be presented just by applying a cas-only access.
- Fact: Most processor addresses are sequential (75%)
- If we had a way of knowing that that the next address is sequential with respect with the current address (current address + 4), then we could only assert cas and make DRAM access fast
- Difficulty?
  - Detecting early in memory access cycle that the next address is in the same row.

ELEC2041 lec31-mem-bus-1.18

Saeid Nooshabadi
 
## ARM Solution to cas-only Access

- ARM address register Instruction:
  - 75% of next addresses are current address +4.




ELEC2041 lec31-mem-bus-1.19

Saeid Nooshabadi
 
## Revised State Transition Diagram

- seq = 1: sequential address
- seq = 0: non-sequential
- mreq = 1 internal operation
- mreq = 0 memory access




ELEC2041 lec31-mem-bus-1.20

Saeid Nooshabadi

 
## DRAM Timing Diagram

- ° Notice the pipelined memory access
- Address is presented 1/2 cycle earlier



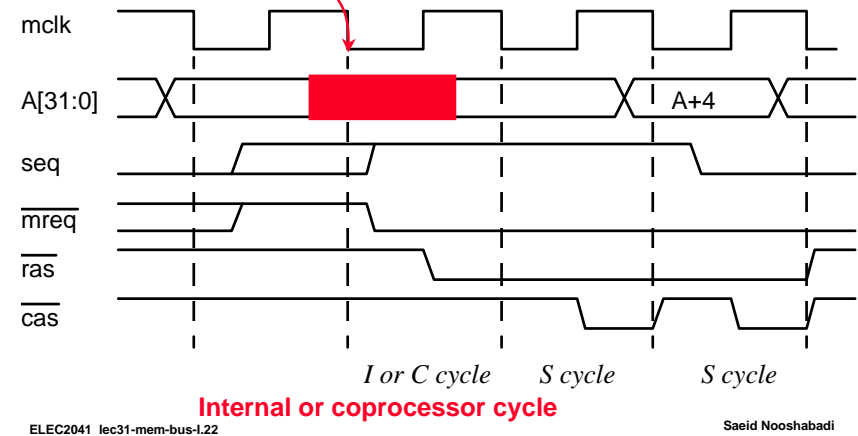
## DRAM Timing Diagram after an Internal Cycle

- ° During internal operations cycles, a memory access cycle can be set up in advance.
- This eliminates the wait (New Cycle) state



## Memory Access Timing Summary

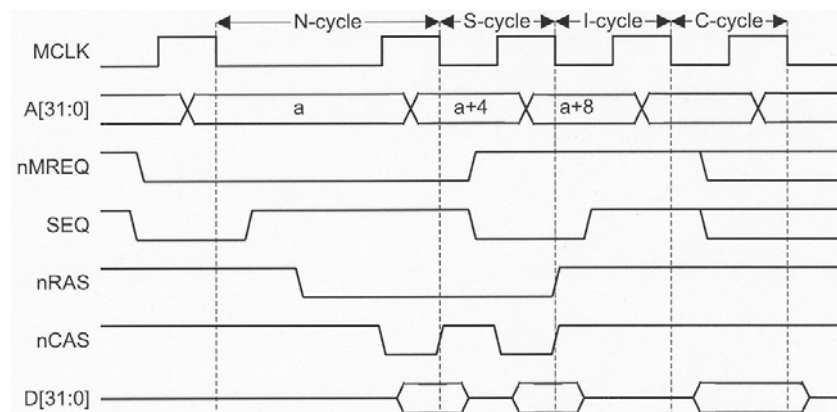

- ° Notice the pipelined memory access
- Address is presented 1/2 cycle earlier

## Reading Material

- ° Steve Furber: ARM System On-Chip; 2nd Ed, Addison-Wesley, 2000, ISBN: 0-201-67519-6. Chapter 8.

## Conclusion

---

- **Memory interfacing can degrade performance**
- **Can improve performance by increasing the clock frequency and allocating differing clock cycles for each memory access type**
- **cas-only accesses in DRAM are 2 to 3 times faster than ras – cas accesses.**